

Lecture #19

AC Currents

1). Consider an AC 10 ampere peak current going through a 10 ohm resistor. The power dissipated is

- (a) 10^3 watts (b) 5×10^2 watts (c) 100 watts (d) 50 watts
-


(2) The units of the quantity $\omega^2 LC$ is

- (a) ohms (b) ohm^2 (c) dimensionless
-

(3) The units of the quantity L/C is

- (a) ohms (b) ohm^2 (c) dimensionless

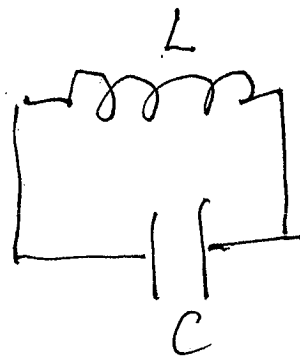(4) An LC circuit with $L = 10^4$ H and a capacitance of



10^{-8} F has a period, T , of oscillation of approximately (Hertz is 1 cycle/sec)

(a) 10^2 Hertz (b) 10^{-2} Hz

(c) 16 Hz

(d) 1600 Hz

(5) In the above example the impedance of the inductor is

(a) $2\pi \cdot 10^6 \Omega$

(b) $10^6 \Omega$

(c) $\frac{10^6}{2\pi} \Omega$

(6) The impedance of the capacitor is (choices above)

(7) An RMS voltage of $10.0V$, with a frequency of $\frac{10^2}{2\pi}$ Hz, is applied across a $100H$ inductor. The power dissipated is



- (a) 1.0 watts (b) 0.5 watts (c) 0


(8) The mean energy stored in the inductor in the previous problem is,

- (a) $10^{-2} J$ (b) $0 J$ (c) $5 \times 10^{-3} J$


(9) An oscillator at $\frac{10^3}{2\pi}$ Hz charges a capacitor of $10^{-9} F$ to $10^{-3} C$ RMS. The peak current through the capacitor is

- (a) $1 A$ (b) $10^{-9} A$ (c) $\sqrt{2} A$ (d) $\sqrt{2} \times 10^{-9} A$

L - C circuit

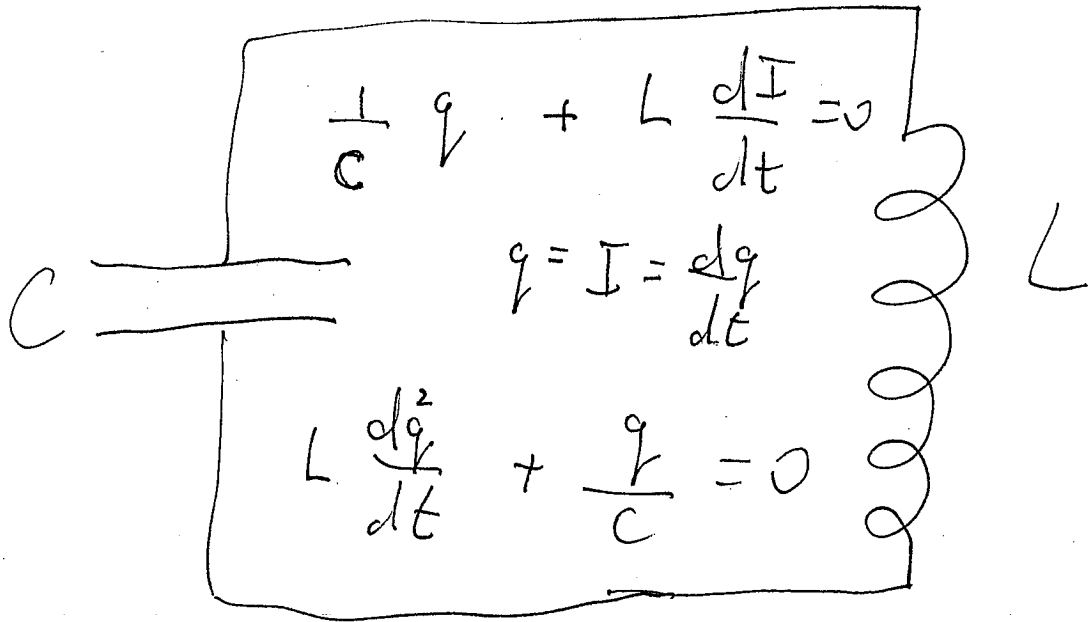

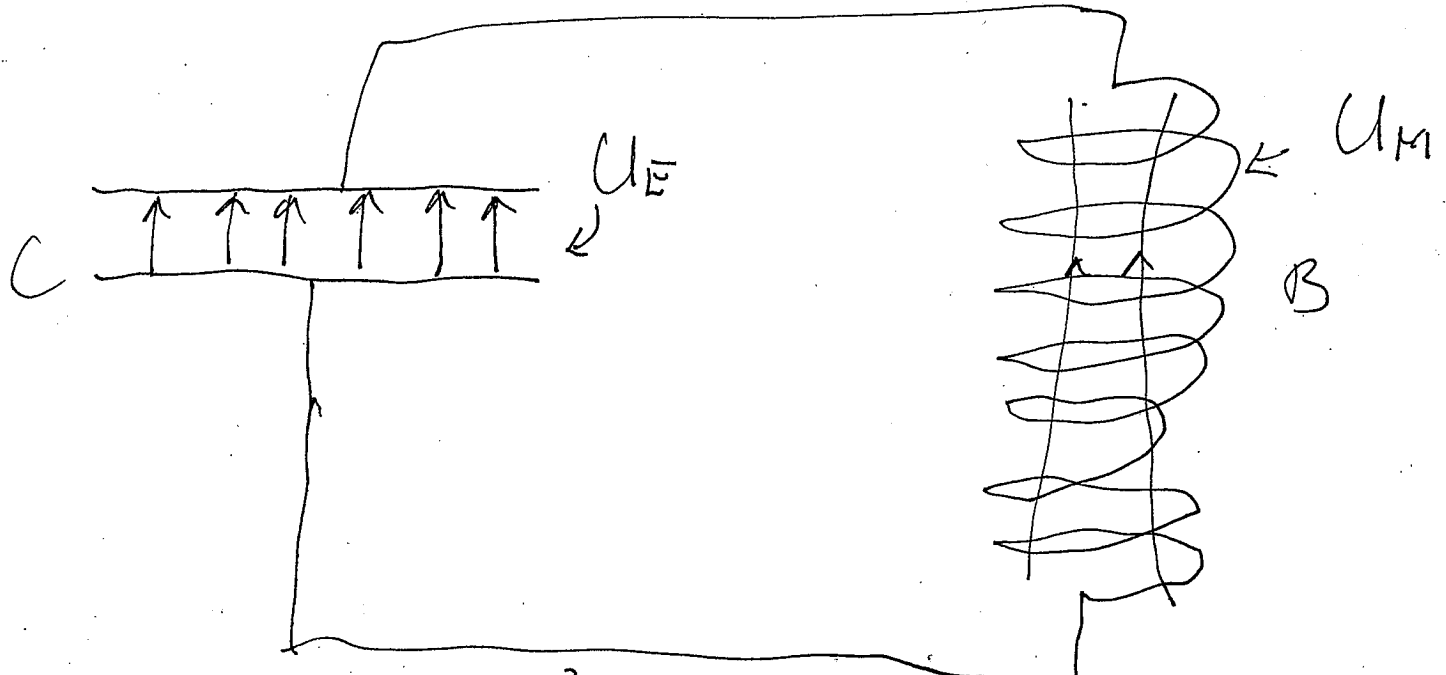
$q = q_0 \sin(\omega_0 t - \phi)$
 $\omega_0 = \frac{1}{\sqrt{LC}}$



$U_E = \epsilon_0 E^2(t) / 2 \equiv \text{electric energy}$

$U_M = B^2(t) / 2\mu_0 \equiv \text{magnetic energy} \quad (4)$

L R C circuit

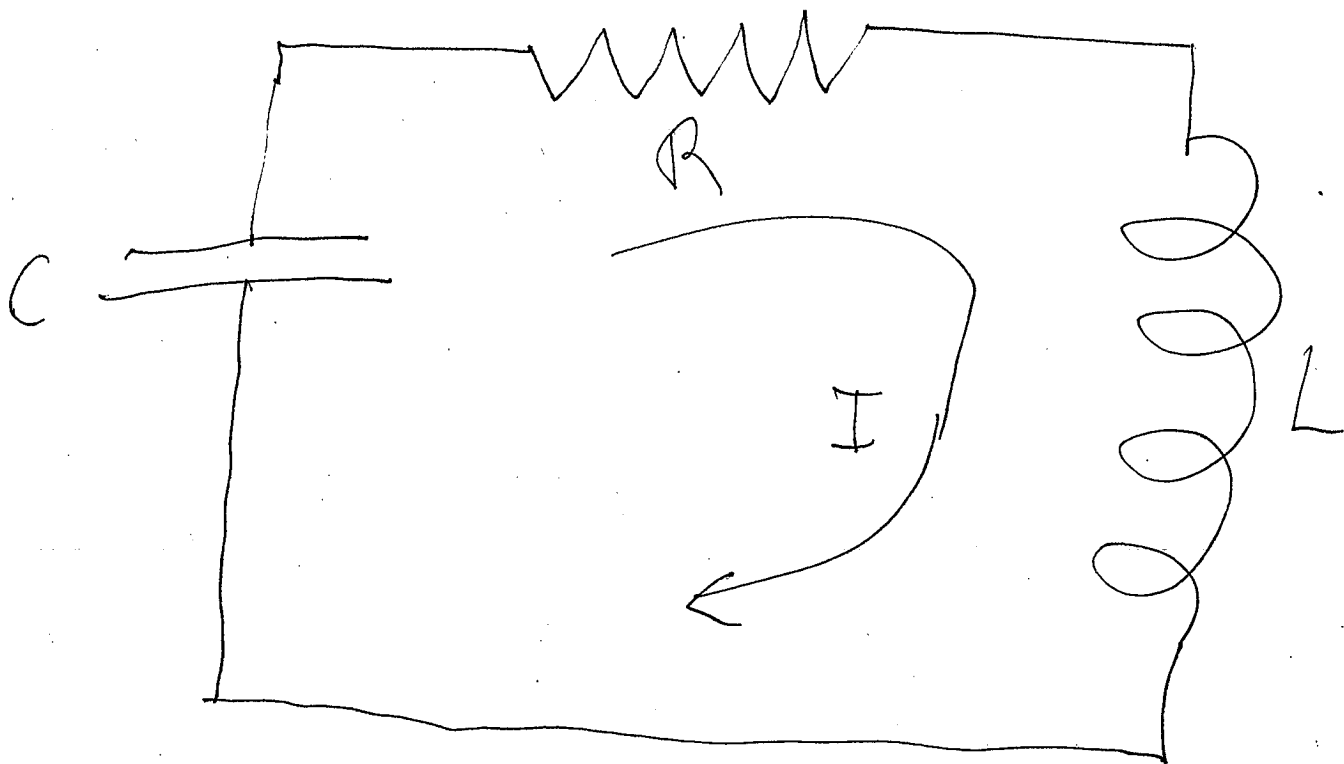


Kirchhoff's Law

$$L \frac{dI}{dt} + \frac{q}{C} + IR = 0$$

$$I = \frac{dq}{dt}$$

$$L \frac{d^2q}{dt^2} +$$

L R C circuit

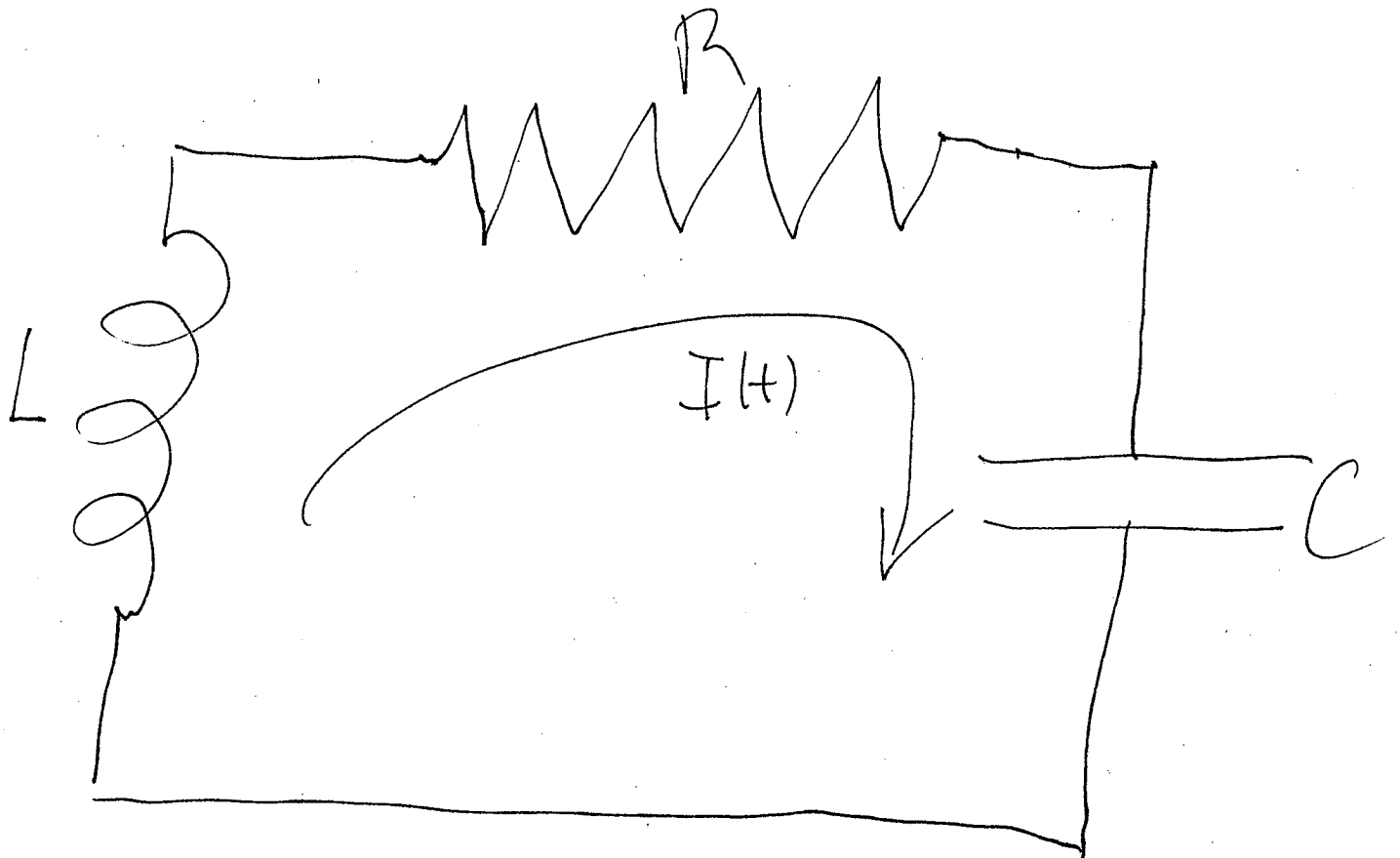

Kirchhoff's Law again

$$L \frac{dI}{dt} + IR + \frac{q}{C} = 0$$

$$I = \frac{dq}{dt}$$

$$L \frac{d^2 q}{dt^2} + \frac{dq}{dt} R + \frac{q}{C} = 0$$

Now the resistor brings in dissipation and electromagnetic energy slowly (if R is small enough) converts to heat energy, and oscillation dies away

$$L \frac{d^2 q}{dt^2} + \frac{dq}{dt} R + \frac{q}{C} = 0$$

($R \leq \sqrt{\frac{L}{C}}$) One can show that decay rate is

$$e^{-\frac{R}{2L}t}$$

Decay rate of AC RLC circuit is

$$\tau = \frac{L}{R} \quad \text{if } R < \sqrt{\frac{L}{C}}$$


For $R > \sqrt{\frac{L}{C}}$, no oscillations

but two different decay rates

$$\tau_C, \tau_L. \quad \text{For } R \gg \sqrt{\frac{L}{C}} \quad \tau_C \rightarrow RC, \quad \tau_L \rightarrow \frac{L}{R} \quad (7)$$

Under damped


$$R < \sqrt{L/C}$$

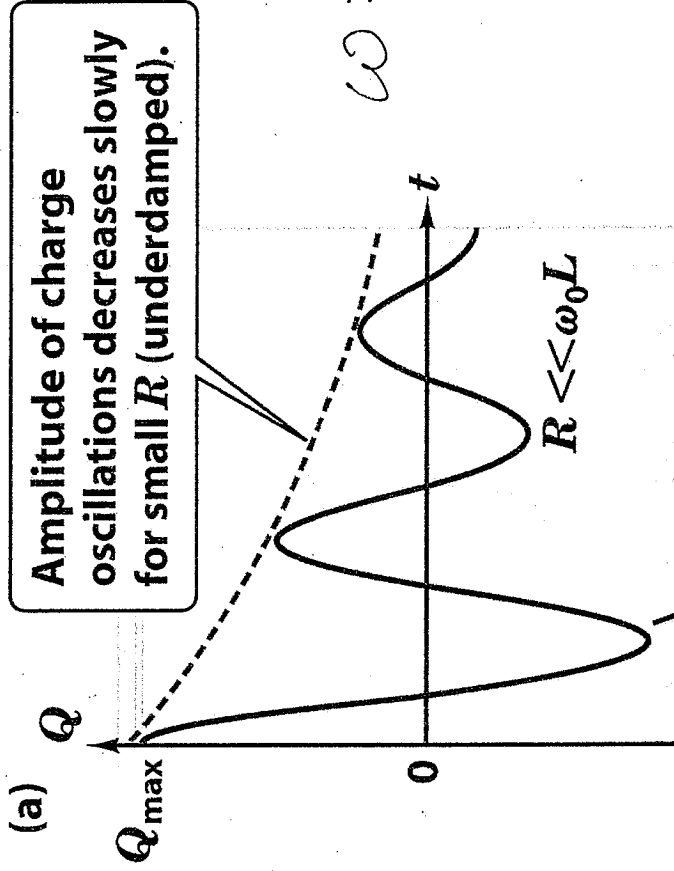

Amplitude of charge oscillations decreases slowly for small R (underdamped).

$$\omega = \left[\omega_0^2 - \left(\frac{R^2}{L^2} C \right) \right]^{1/2}$$

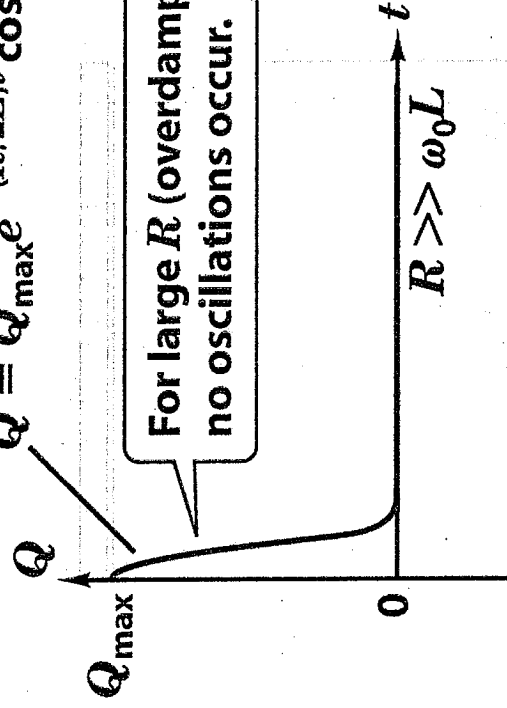(b) $Q = Q_{\max} e^{-(R/2L)t} \cos \omega_d t$



For large R (overdamped), no oscillations occur.

Overdamped

$$R > \sqrt{L/C}$$

two characteristic damping time


$$Q = Q_1 \exp(-t/\tau_1) + Q_2 \exp(-t/\tau_2)$$

$$\tau_1 \rightarrow L/R \quad \text{when } \frac{R^2 C}{L} > 1$$

$$\tau_2 \rightarrow RC$$

Figure 32-20 Physics for Engineers and Scientists 3/e © 2007 W. W. Norton & Company, Inc.

AC LRC circuit

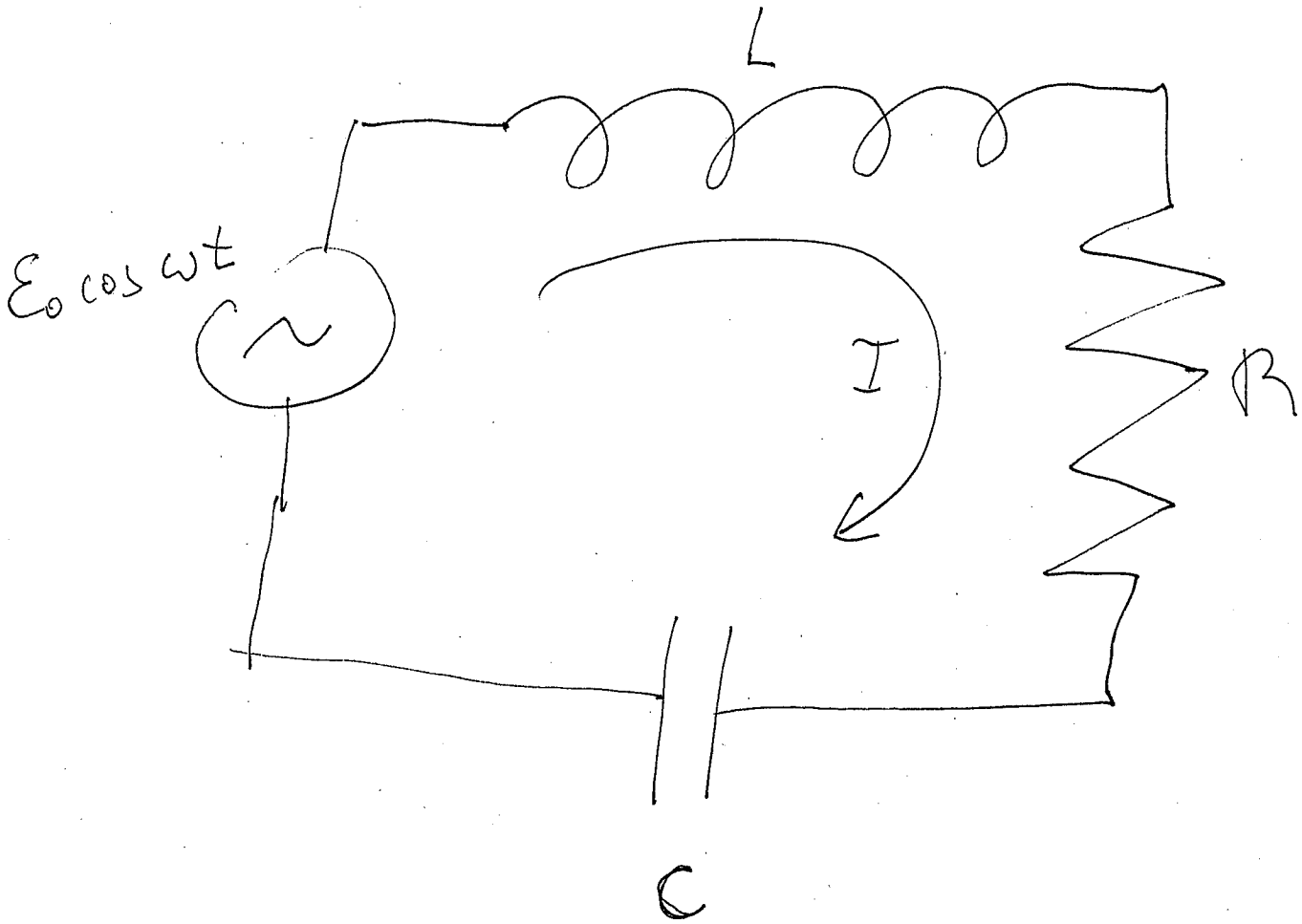

Khirchoff's voltage Law

$$-E_0 \cos \omega t + L \frac{dI}{dt} + IR + \frac{q}{C} = 0$$

Two different solutions

(a) Transient (homogeneous) solution: Eventually decays

(b) Particular Solution: With E_0 finite remains as long as E_0 present (8)

$$\mathcal{E}_0 \cos \omega t = L \frac{dI}{dt} + IR + \frac{q}{C}$$

Forced oscillation

$$I = I_0 \cos(\omega t + \phi)$$

↑
↑
 amplitude phase

$$-\frac{\pi}{2} < \phi < \frac{\pi}{2}$$

$$0 < \phi \leq \frac{\pi}{2}$$

Capacitive-like circuit, current leads voltage

$$-\frac{\pi}{2} \leq \phi < 0$$

Inductive-like circuit, current lags voltage

$$E_0 \cos \omega t = L \frac{dI}{dt} + IR + \frac{q}{C} \quad (a)$$

If $I(t) = I_0 \cos(\omega t + \phi) \quad (b)$

then $q(t) = \frac{I_0}{\omega} \sin(\omega t + \phi) \quad (c)$

(note then $\frac{dq(t)}{dt} = I_0 \cos(\omega t + \phi) = I(t)$)

$$\frac{dI}{dt} = -\omega I_0 \sin(\omega t + \phi) \quad (d)$$

Substitute b, c, d into (a)

we obtain

$$E_0 \cos \omega t = I_0 \left[\left(\frac{1}{\omega C} - \omega L \right) \sin(\omega t + \phi) + R \cos(\omega t + \phi) \right]$$

$$\mathcal{E}_0 \cos \omega t = I_0 \left[\left(\frac{1}{\omega C} - \omega L \right) \sin(\omega t + \phi) + R \cos(\omega t + \phi) \right] \quad (I)$$

Equation (I) has a unique solution for I_0 and ϕ (please verify the stated solution as exercise)

$$I_0 = \frac{\mathcal{E}_0}{X_{\text{total}}} ; Z = \left[\left(\frac{1}{\omega C} - \omega L \right)^2 + R^2 \right]^{1/2}$$

$$\phi = \tan^{-1} \left(\frac{\frac{1}{\omega C} - \omega L}{R} \right)$$

If $\frac{1}{\omega C} > \omega L$, $\phi > 0$

inductive
(low frequency)

If $\frac{1}{\omega C} < \omega L$, $\phi < 0$

capacitive
(high frequency)

If $\frac{1}{\omega C} = \omega L$, $\phi = 0$

purely resistive
resonance.

For a given voltage, \mathcal{E}_0
 and fixed resistance,
 the largest current, I_0 ,
 comes when the resonance condition
 is fulfilled $\omega = \omega_0 \equiv \frac{1}{\sqrt{LC}}$

$$I_0 = \frac{\mathcal{E}_0}{\left[R^2 + \left(\frac{1}{\omega C} - \omega L \right)^2 \right]^{1/2}}$$

Power delivered to
 resistor (load)

$$P = \frac{I_0^2 R}{2} = \frac{\mathcal{E}_0^2}{2} \frac{R}{\left[R^2 + \left(\frac{1}{\omega C} - \omega L \right)^2 \right]}$$

clearly largest when $\frac{1}{\omega C} - \omega L = 0$

Let us look near resonance

$$\omega = \omega_0 + \delta\omega$$

$$P = \frac{I_0^2 R}{2} = \frac{\epsilon_0^2}{2} \frac{R}{\left[R^2 + \left(\frac{1}{(\omega_0 + \delta\omega)C} - (\omega_0 + \delta\omega)L \right)^2 \right]}$$

$$\left(\frac{1}{(\omega_0 + \delta\omega)C} - (\omega_0 + \delta\omega)L \right) \approx \left(\frac{1}{\omega_0 C} \left(1 - \frac{\delta\omega}{\omega_0} \right) - \omega_0 L \left(1 + \frac{\delta\omega}{\omega_0} \right) \right)$$

$$\delta\omega = \omega - \omega_0; \quad \omega_0^2 = \frac{1}{LC}$$

$$\frac{1}{\omega_0 C} - \omega_0 L = \sqrt{\frac{L}{C}} - \sqrt{\frac{L}{C}} = 0$$

Then consider next terms

$$\rightarrow \frac{1}{\omega_0 C} \frac{\delta\omega}{\omega_0} - \omega_0 L \frac{\delta\omega}{\omega_0} = 2L \delta\omega$$

$$P = \frac{\epsilon_0^2}{2} \frac{R}{\left[R^2 + 4L^2 \delta\omega^2 \right]}$$

$$P = \frac{E_0^2}{2} \frac{R}{[R^2 + 4L^2 \delta \omega^2]}$$

$$= \frac{E_0^2}{2R} \frac{1}{\left[1 + \frac{4L^2 \omega_0^2}{R^2} \frac{\delta \omega^2}{\omega_0^2}\right]}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$= \frac{E_0}{2R_0} \frac{1}{\left[1 + \frac{4L}{CR^2} \frac{\delta \omega^2}{\omega_0^2}\right]}$$

$$P = \frac{E_0^2}{2R_0} \frac{1}{\left[1 + 4Q^2 \frac{(\omega - \omega_0)^2}{\omega_0^2}\right]}$$

$$Q = \frac{(L/C)^{1/2}}{R} \equiv \text{Quality Factor of Circuit}$$

When $\omega - \omega_0 = \frac{\omega_0}{2Q}$ power received by load is down by $\frac{1}{2}$ (1/2)

r - receiver
 t - transmitter


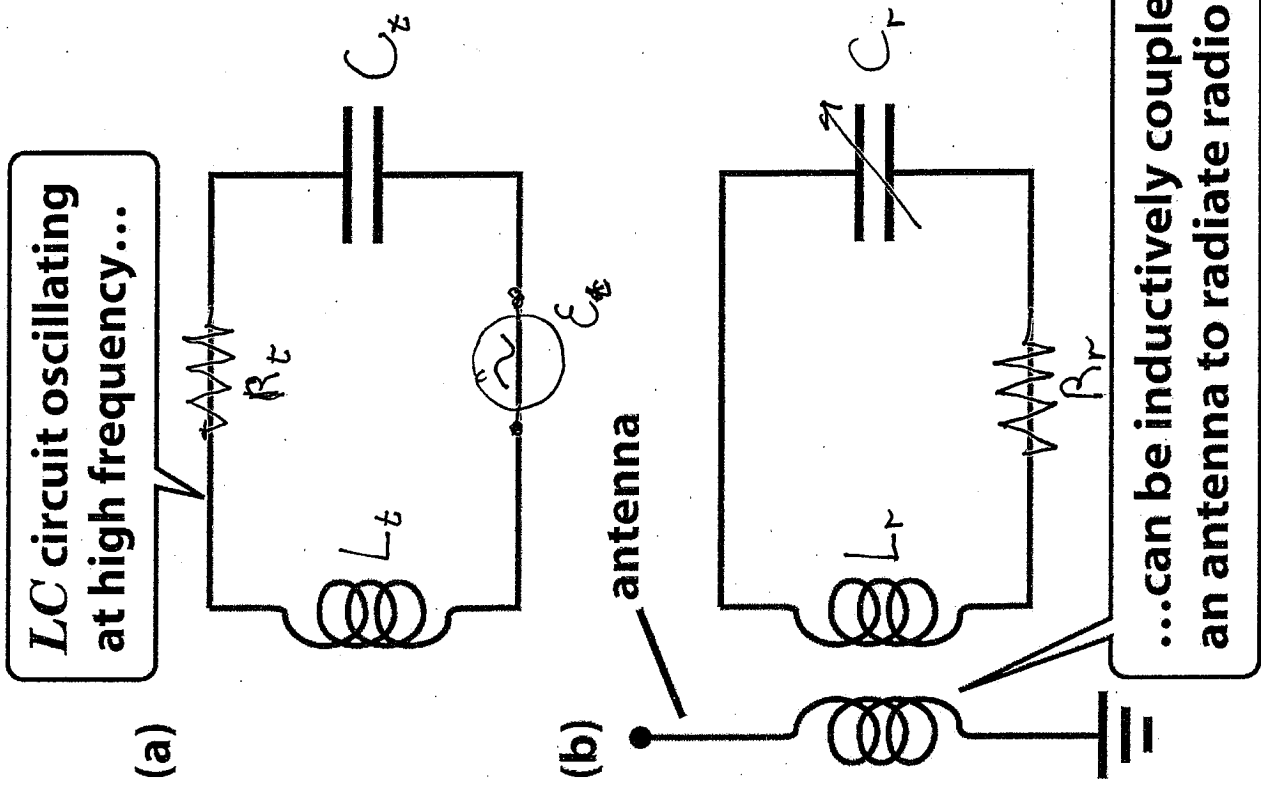


Figure 32-17 Physics for Engineers and Scientists 3/e
 © 2007 W. W. Norton & Company, Inc.

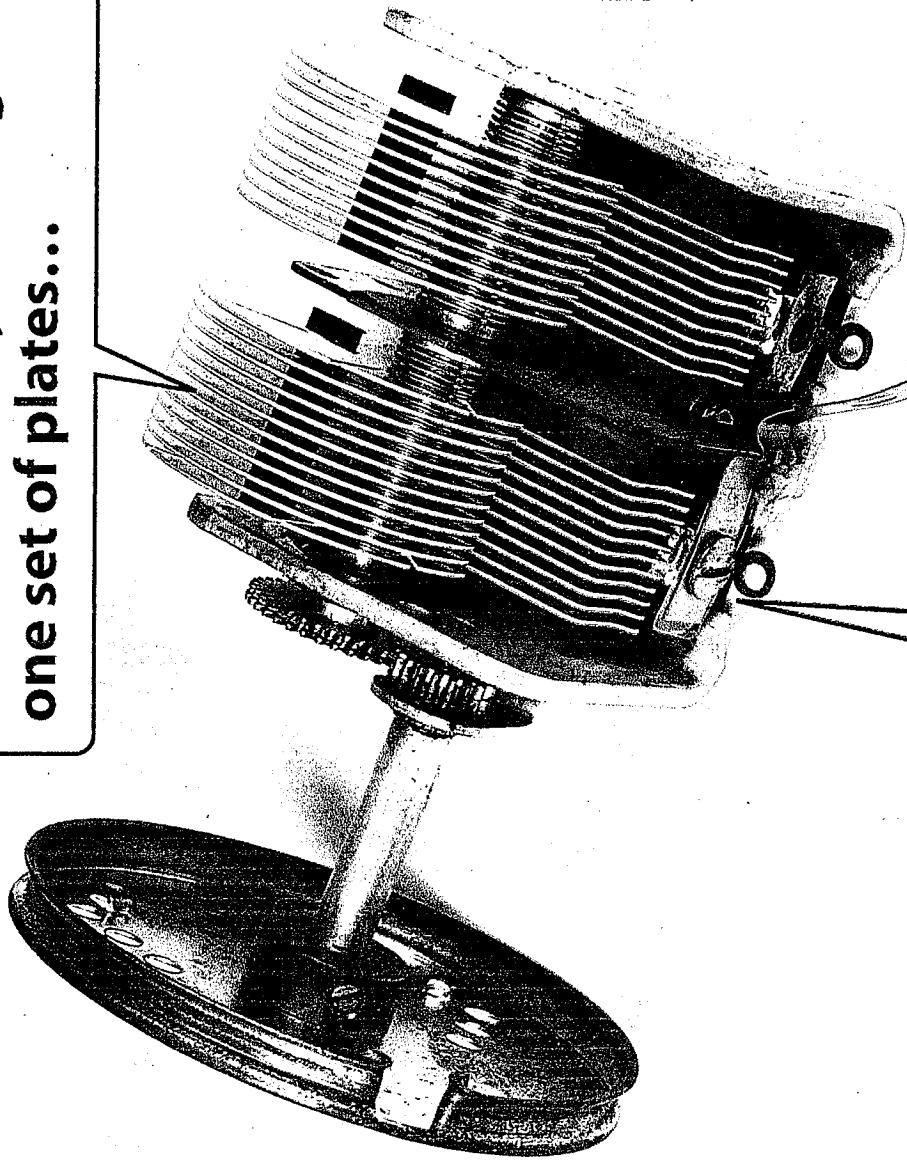**Value of variable capacitor
is controlled by moving
one set of plates...**



**...relative to a fixed set of
plates, changing area of overlap.**

Figure 32-18 Physics for Engineers and Scientists 3/e
Loren Winters/Visuals Unlimited