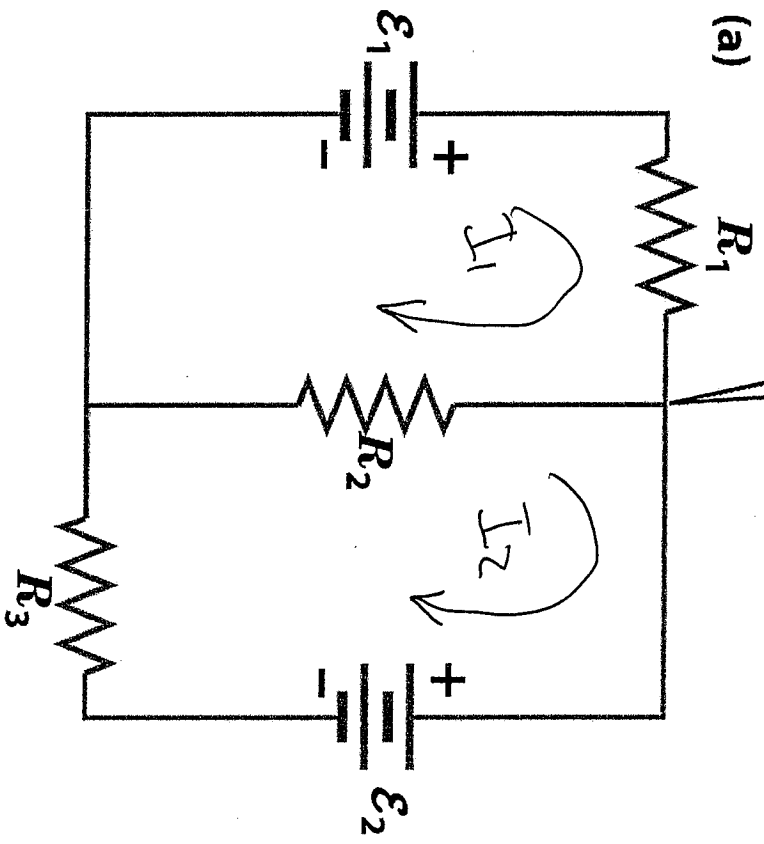



Lecture # 16

DC circuits

For this two-loop circuit...




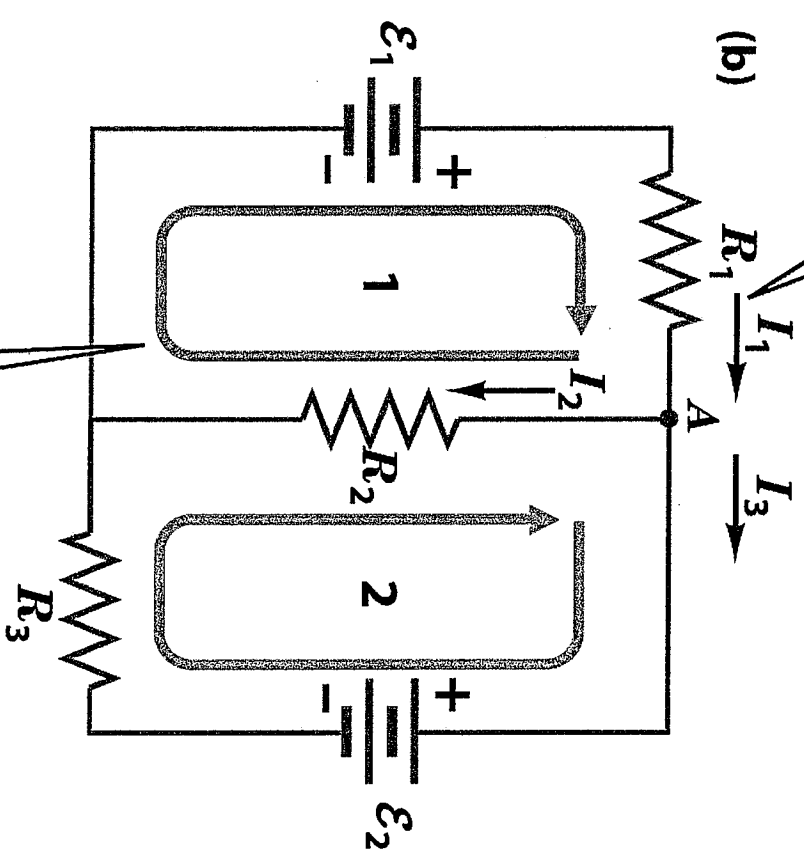...we first label and draw arrows for the three separate branch currents...



...and then choose a starting point and direction to go around each loop.

Two loop active circuit

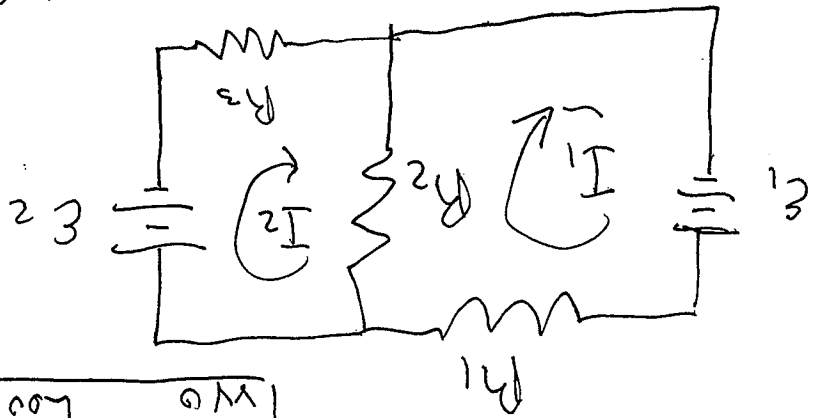

$$-E_1 + I_1 R_1 + (I_1 - I_2) R_2 = 0$$

$$E_2 + I_2 R_3 + (I_2 - I_1) R_2 = 0$$

$$(R_1 + R_2) I_1 - R_2 I_2 = E_1$$

$$-R_2 I_1 + (R_2 + R_3) I_2 = -E_2$$

$$I_1 = \frac{\begin{vmatrix} E_1 & -E_2 \\ R_1 + R_2 & -R_2 \end{vmatrix}}{\begin{vmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{vmatrix}}$$

$$I_2 = \frac{\begin{vmatrix} R_1 + R_2 & E_1 \\ -R_2 & -E_2 \end{vmatrix}}{\begin{vmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{vmatrix}}$$

$$I_1 = \frac{(R_1 + R_2) E_1 - R_2 E_2}{(R_1 + R_2)(R_2 + R_3) - R_2^2}$$

$$I_2 = \frac{R_2 E_1 - E_2 (R_1 + R_2)}{(R_1 + R_2)(R_2 + R_3) - R_2^2}$$

Note:  $(R_1 + R_2)(R_2 + R_3) - R_2^2 = R_1 R_2 + R_2 R_3 + R_2 R_1 + R_2 R_3$

For a complicated circuit with several loops and branches...

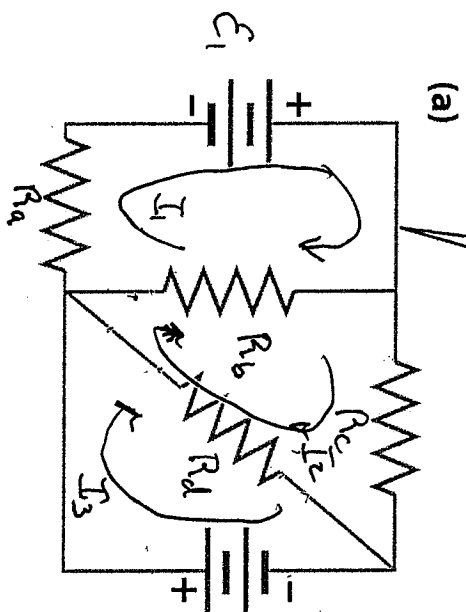


Figure 28-16 Physics for Engineers and Scientists 3/e  
© 2007 W. W. Norton & Company, Inc.

$$-\mathcal{E}_1 + R_b(I_1 - I_2) + R_a I_1 = 0$$

$$I_2 R_c + R_d(I_2 - I_3) + R_b(I_2 - I_1) = 0$$

$$-\mathcal{E}_2 + R_d(I_3 - I_2) = 0$$

Unknowns  $I_1, I_2, I_3$

$$(R_b + R_a)I_1 - R_b I_2 + 0 I_3 = \mathcal{E}_1$$

$$-R_b I_1 + (R_b + R_d + R_c)I_2 - R_d I_3 = 0$$

$$0 I_1 - R_d I_2 + R_d I_3 = \mathcal{E}_2$$

Can be solved by methods of linear algebra

For a complicated circuit with several loops and branches...

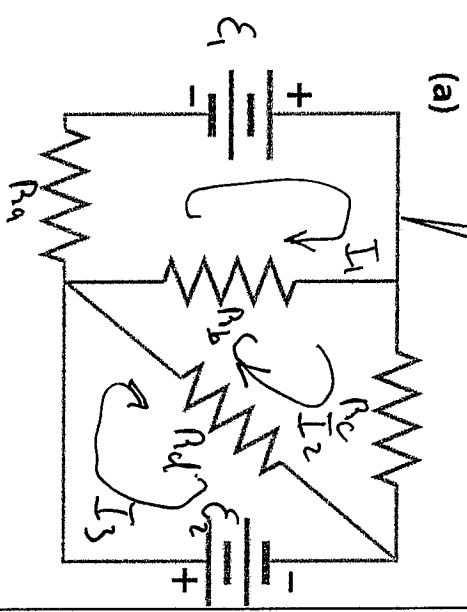


Figure 28-16 Physics for Engineers and Scientists 3/e © 2007 W. W. Norton & Company, Inc.

$$Q_{11} X_1 + Q_{12} X_2 + Q_{13} X_3 = Y_1$$

$$Q_{21} X_1 + Q_{22} X_2 + Q_{23} X_3 = Y_2$$

$$Q_{31} X_1 + Q_{32} X_2 + Q_{33} X_3 = Y_3$$

$$X_1 = \frac{Y_1 \begin{vmatrix} Q_{22} & Q_{23} \\ Q_{32} & Q_{33} \end{vmatrix} - Y_2 \begin{vmatrix} Q_{12} & Q_{13} \\ Q_{32} & Q_{33} \end{vmatrix} + Y_3 \begin{vmatrix} Q_{12} & Q_{13} \\ Q_{22} & Q_{23} \end{vmatrix}}{\begin{vmatrix} Q_{11} & Q_{12} & Q_{13} \\ Q_{21} & Q_{22} & Q_{23} \\ Q_{31} & Q_{32} & Q_{33} \end{vmatrix}}$$

$$\begin{vmatrix} Q_{11} & Q_{12} & Q_{13} \\ Q_{21} & Q_{22} & Q_{23} \\ Q_{31} & Q_{32} & Q_{33} \end{vmatrix}$$

$$X_2 = \frac{-Y_1 \begin{vmatrix} Q_{11} & Q_{13} \\ Q_{31} & Q_{33} \end{vmatrix} + Y_2 \begin{vmatrix} Q_{11} & Q_{13} \\ Q_{21} & Q_{23} \end{vmatrix} - Y_3 \begin{vmatrix} Q_{11} & Q_{13} \\ Q_{21} & Q_{23} \end{vmatrix}}{\begin{vmatrix} Q_{11} & Q_{12} & Q_{13} \\ Q_{21} & Q_{22} & Q_{23} \\ Q_{31} & Q_{32} & Q_{33} \end{vmatrix}}$$

$$X_3 = \frac{Y_1 \begin{vmatrix} Q_{11} & Q_{12} \\ Q_{21} & Q_{22} \end{vmatrix} - Y_2 \begin{vmatrix} Q_{11} & Q_{12} \\ Q_{31} & Q_{32} \end{vmatrix} + Y_3 \begin{vmatrix} Q_{11} & Q_{12} \\ Q_{21} & Q_{22} \end{vmatrix}}{\begin{vmatrix} Q_{11} & Q_{12} & Q_{13} \\ Q_{21} & Q_{22} & Q_{23} \\ Q_{31} & Q_{32} & Q_{33} \end{vmatrix}}$$

$$X_1 = \frac{Y_1 \begin{vmatrix} Q_{22} & Q_{23} \\ Q_{32} & Q_{33} \end{vmatrix} - Y_2 \begin{vmatrix} Q_{12} & Q_{13} \\ Q_{32} & Q_{33} \end{vmatrix} + Y_3 \begin{vmatrix} Q_{12} & Q_{13} \\ Q_{22} & Q_{23} \end{vmatrix}}{\begin{vmatrix} Q_{11} & Q_{12} & Q_{13} \\ Q_{21} & Q_{22} & Q_{23} \\ Q_{31} & Q_{32} & Q_{33} \end{vmatrix}}$$

$$X_2 = \frac{-Y_1 \begin{vmatrix} Q_{11} & Q_{13} \\ Q_{31} & Q_{33} \end{vmatrix} + Y_2 \begin{vmatrix} Q_{11} & Q_{13} \\ Q_{21} & Q_{23} \end{vmatrix} - Y_3 \begin{vmatrix} Q_{11} & Q_{13} \\ Q_{21} & Q_{23} \end{vmatrix}}{\begin{vmatrix} Q_{11} & Q_{12} & Q_{13} \\ Q_{21} & Q_{22} & Q_{23} \\ Q_{31} & Q_{32} & Q_{33} \end{vmatrix}}$$

$$X_3 = \frac{Y_1 \begin{vmatrix} Q_{11} & Q_{12} \\ Q_{21} & Q_{22} \end{vmatrix} - Y_2 \begin{vmatrix} Q_{11} & Q_{12} \\ Q_{31} & Q_{32} \end{vmatrix} + Y_3 \begin{vmatrix} Q_{11} & Q_{12} \\ Q_{21} & Q_{22} \end{vmatrix}}{\begin{vmatrix} Q_{11} & Q_{12} & Q_{13} \\ Q_{21} & Q_{22} & Q_{23} \\ Q_{31} & Q_{32} & Q_{33} \end{vmatrix}}$$

[3]

Let us solve for  $I_1$

For a complicated circuit with several loops and branches...


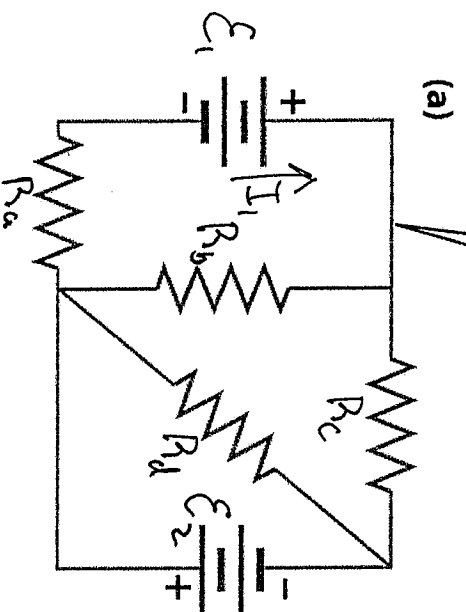


Figure 28-16 Physics for Engineers and Scientists 3/e © 2007 W. W. Norton & Company, Inc.

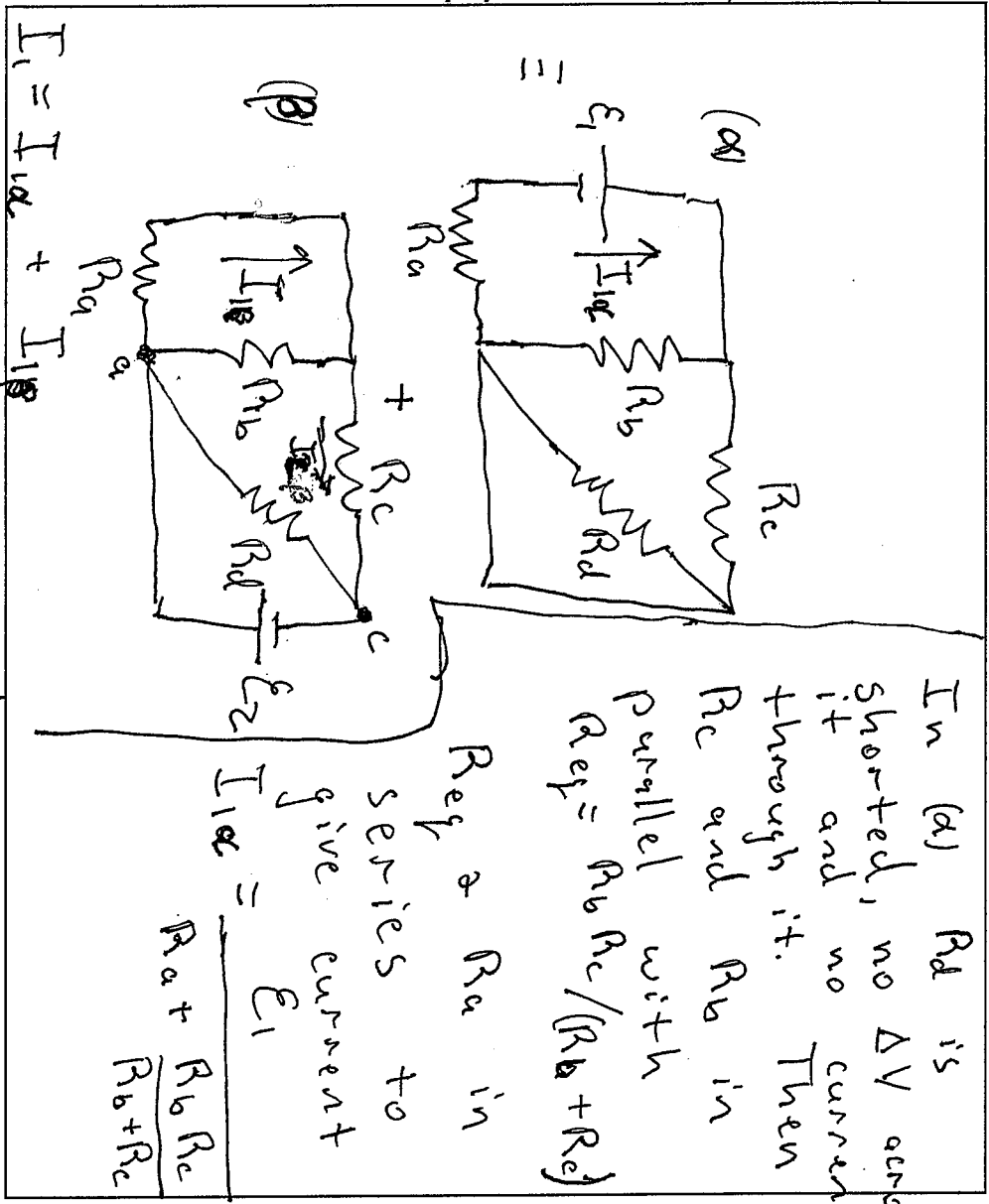

$I_1$  in (a)  $R_d$  is shorted, no  $\Delta V$  across it and no current through it. Then  $R_c$  and  $R_b$  in parallel with  $R_{eq} = R_b R_c / (R_b + R_c)$

$R_{eq}$  &  $R_a$  in series to give current

$$I_{1a} = \frac{E_1}{R_a + \frac{R_b R_c}{R_b + R_c}}$$

$$I_1 = I_{1a} + I_{1b}$$

$I_1$  (B)

The voltage drop produces a current through  $R_c$  given by

$$I_{1b} = \frac{E_2}{R_c + R_b}$$

$$I_1 = \frac{E_2 R_b}{R_c + R_b}$$

(A)

For a complicated circuit with several loops and branches...



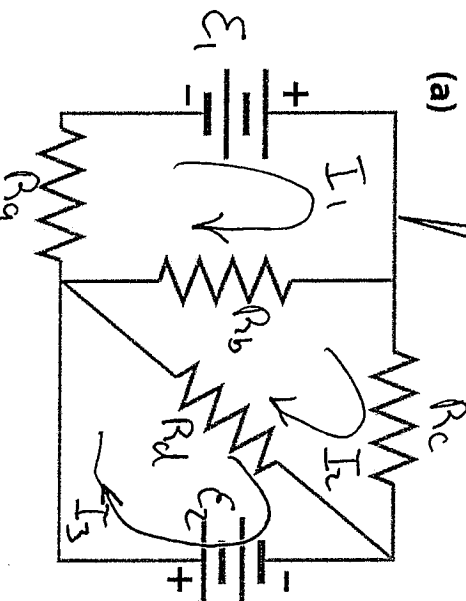


Figure 28-16 Physics for Engineers and Scientists 3/e  
© 2007 W. W. Norton & Company, Inc.

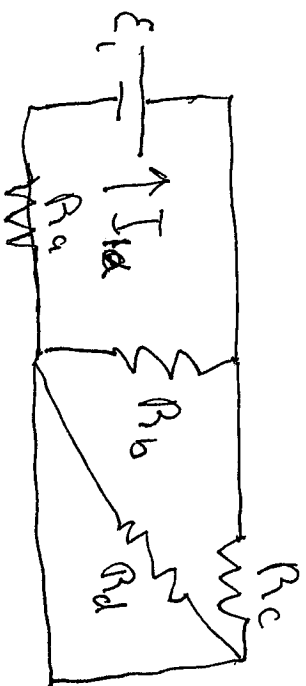
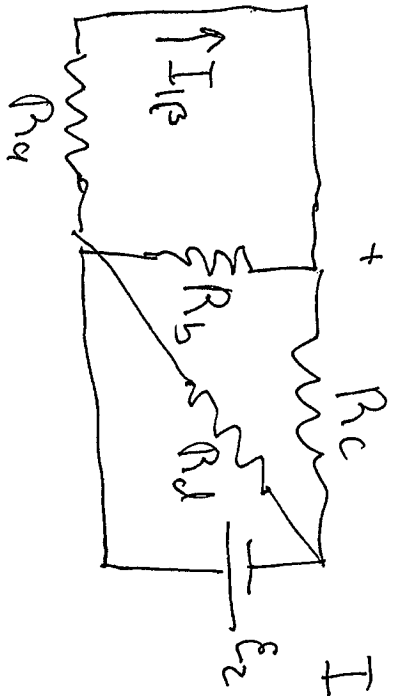
$$I_{12} = \frac{\mathcal{E}_1}{R_a + \frac{R_b R_c}{R_b + R_c}}$$



$$I_{13} = \frac{\mathcal{E}_2 R_b}{R_c R_a + R_c R_b + R_b R_a}$$

$$I_1 = I_{12} + I_{23} = \frac{\mathcal{E}_1 (R_b + R_c)}{R_a R_b + R_a R_c + R_c R_b} + \frac{\mathcal{E}_2 R_b}{R_c R_a + R_c R_b + R_b R_a}$$


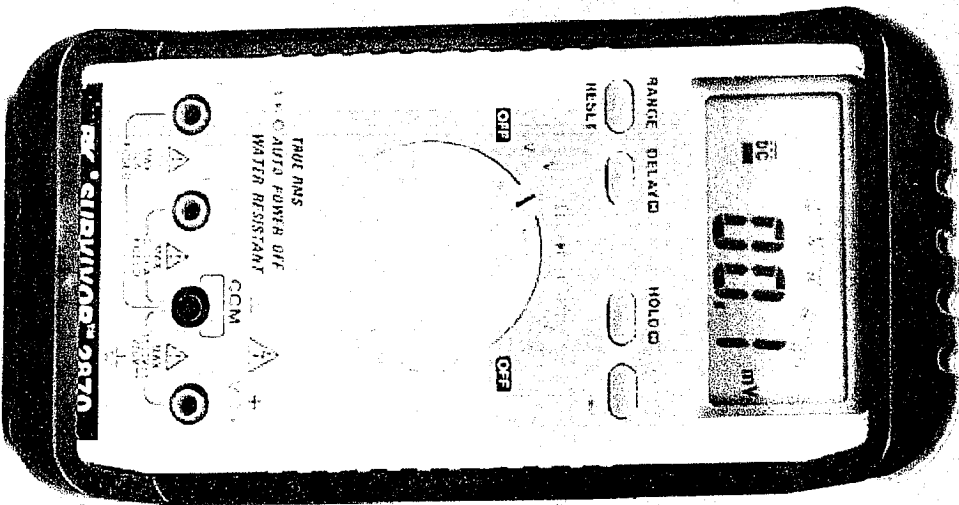


Figure 28-22 Physics for Engineers and Scientists 3/e  
Loren Winters/Visuals Unlimited

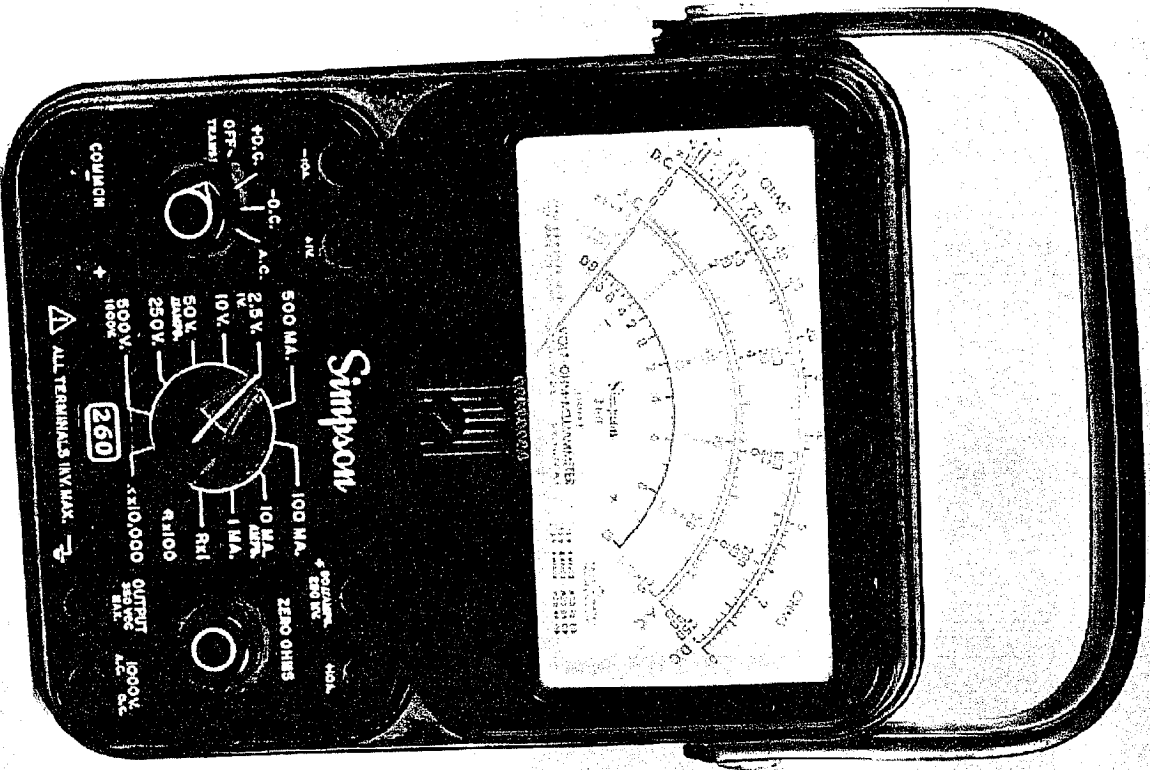

Internal Battery resistance,  $R_{in}$

$$I_{load} = \frac{\mathcal{E}}{R_{load}}, \quad R_{in} = 0$$

$$I_{actual (load)} = \frac{\mathcal{E}}{R_{load} + R_{in}}$$

Ammeter must be placed in path of current.

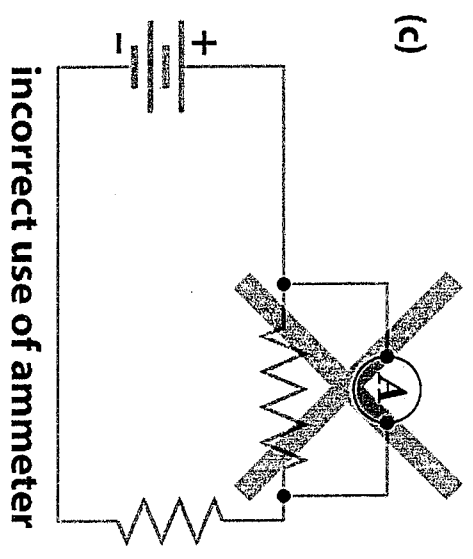
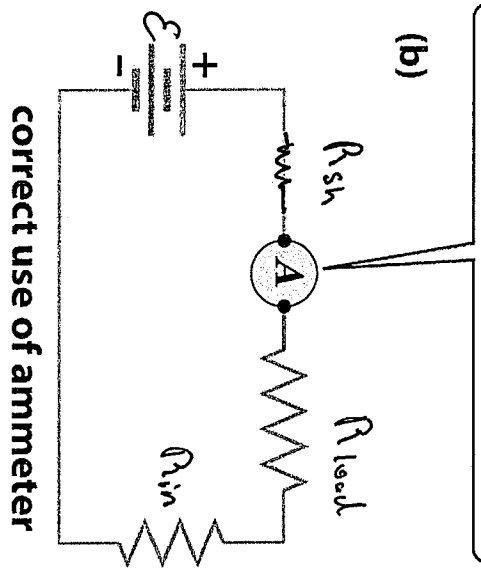
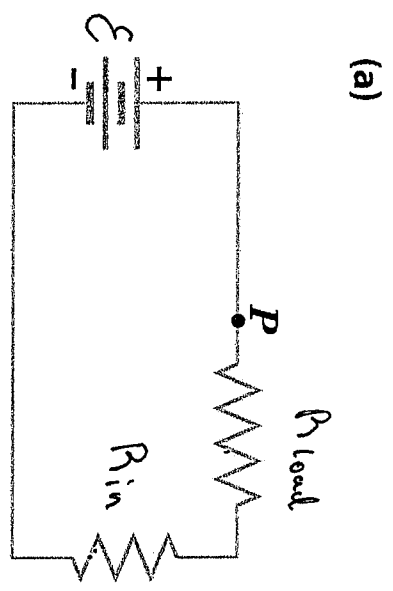


Figure 28-23 Physics for Engineers and Scientists 3/e  
© 2007 W. W. Norton & Company, Inc.

$R_{in} \equiv$  internal  
 $R_{sh} \equiv$  internal

We need to get an accurate reading of


resistance of battery  
resistance of ammeter

ammeter

(a)  $R_{sh} \ll R_{load}$

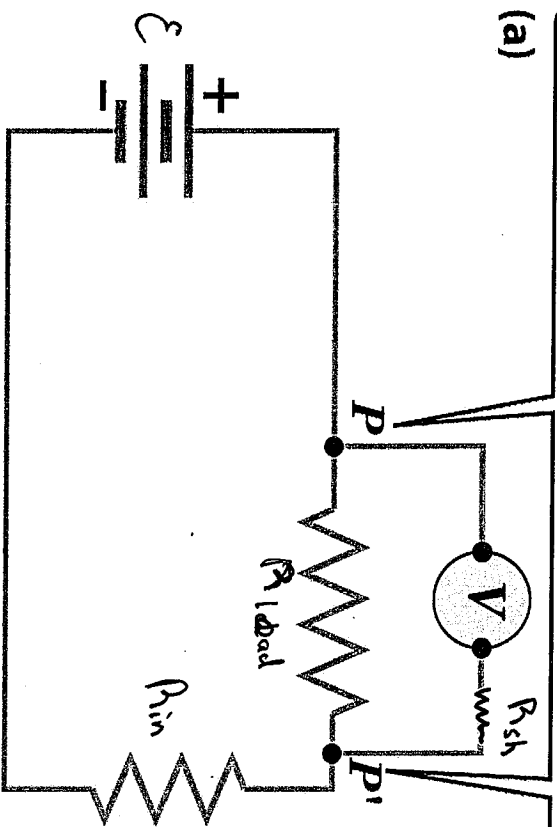(b)  $R_{sh} \gg R_{load}$


Voltmeter is connected to measure potential difference between two points.



**correct use of voltmeter**

To get accurate reading on voltmeter, we need

(a)  $R_{sh} \ll R_{load}$

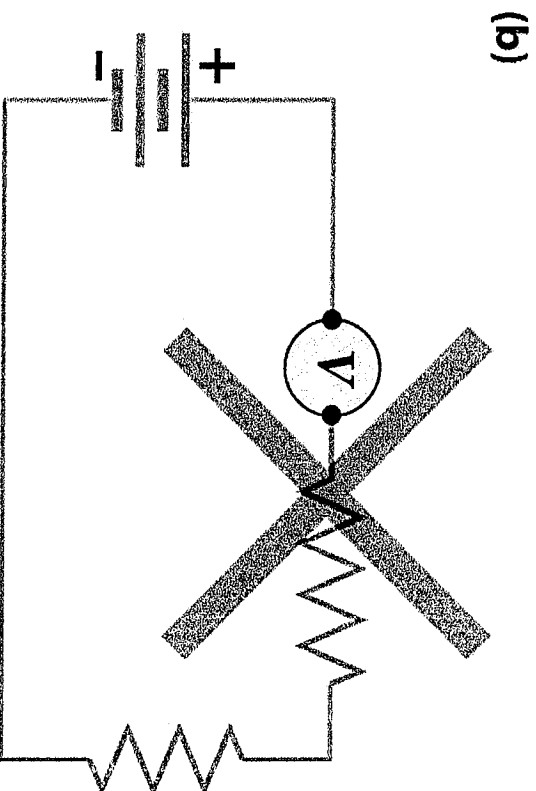

**incorrect use of voltmeter**

(b)  $R_{sh} \gg R_{load}$

Figure 28-24 Physics for Engineers and Scientists 3/e  
© 2007 W. W. Norton & Company, Inc.

Energy  $\Delta E$  dissipation in resistor in time  $\Delta t$

$$\Delta E = V \Delta q$$

Power  $P = \Delta E / \Delta t = V \Delta q / \Delta t$

or

$$P = V dq/dt = VI = I^2 R = V^2/R$$

Handwritten notes:

$$P = VI$$

$$V = IR$$

$$I = \frac{V}{R}$$

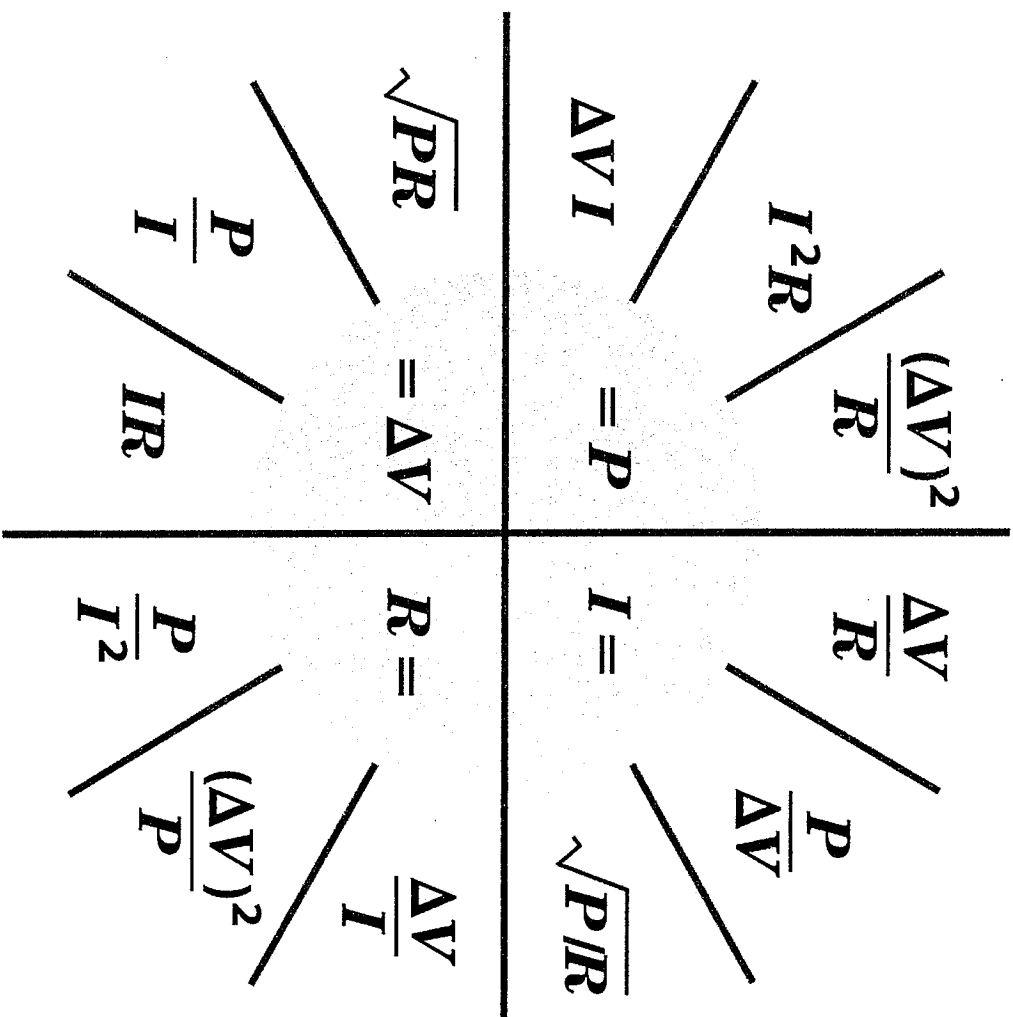


Figure 28-18 Physics for Engineers and Scientists 3/e © 2007 W.W. Norton & Company, Inc.