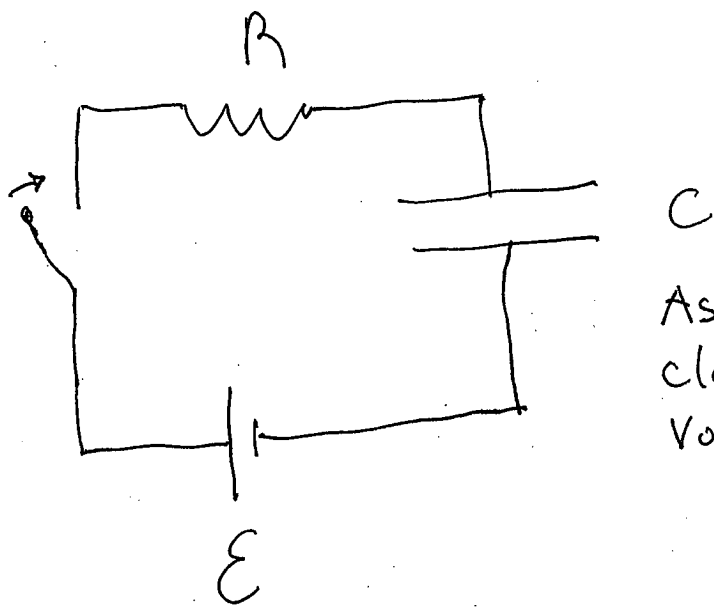


Lecture # 17

RC circuits




As soon as we close switch, Kirchhoff's voltage law holds:

Initially a switch is open and a capacitor is uncharged. The switch is suddenly closed. Immediately afterward, before any charge can flow through the battery, the voltage across the capacitor is:

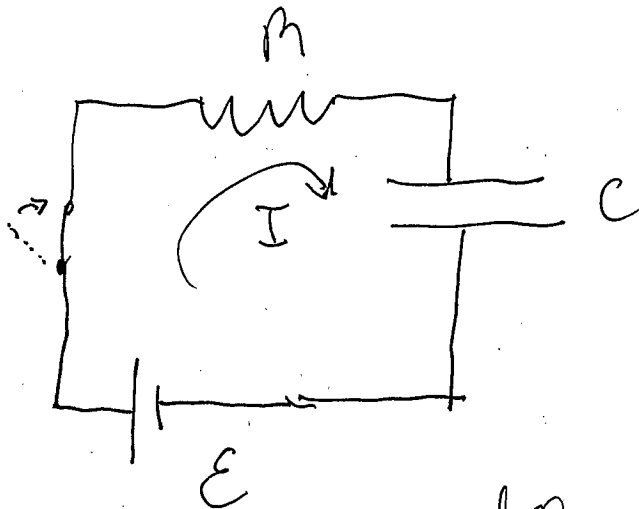(a) 0 (b) E

If after we close the switch and wait long enough, the voltage across the battery is?

Kirchoff's voltage law
applies to an RC circuit



$$I = \frac{dQ}{dt}$$

$$-E + IR + \frac{Q}{C} = 0$$

or

$$-E + R \frac{dQ}{dt} + \frac{Q}{C} = 0$$

Standard Form

$$R \frac{dQ}{dt} + \frac{Q}{C} = E$$

What is solution to ($\mathcal{E}=0$)
equation?

$$R \frac{dQ}{dt} + \frac{Q}{C} = 0$$

$$\frac{dQ}{Q} = - \frac{dt}{RC}$$

$$\ln Q = - \frac{t}{RC} + \text{Const}$$

$$\text{let Const} = \ln Q_0$$

$$\ln Q = - \frac{t}{RC} + \ln Q_0$$

$$\ln Q - \ln Q_0 = \ln (Q/Q_0)$$

$$\ln \left(\frac{Q}{Q_0} \right) = - \frac{t}{RC}$$

$$Q = Q_0 \exp(-t/RC)$$

Mathematically: $\ln Q_0$ constant of integration
of an integral

Special solution, Q_I , to equation:

$$R \frac{dQ}{dt} + \frac{Q}{C} = E$$

$$Q_I = CE \quad \left(\text{or inhomogeneous solution} \right)$$

Homogeneous solution, Q_H

$$R \frac{dQ_H}{dt} + \frac{Q_H}{C} = 0$$

$$Q_H(t) = Q_0 \exp\left(-\frac{t}{RC}\right) \equiv Q_0 \exp\left(-\frac{t}{\tau}\right)$$

$\tau \equiv RC \equiv$ time constant of RC circuit.

General Solution

$$Q(t) = Q_0 \exp\left(-\frac{t}{RC}\right) + EC$$

$$0 = Q(t=0) = Q_0 + EC; \quad Q_0 = -EC$$

Charging a capacitor

Suppose initially there is no charge on capacitor:

General Solution to

circuit equation is:

$$Q(t) = Q_0 \exp\left(-\frac{t}{RC}\right) + \epsilon C$$

$Q(t) \equiv$ charge on capacitor:

What must Q_0 be?


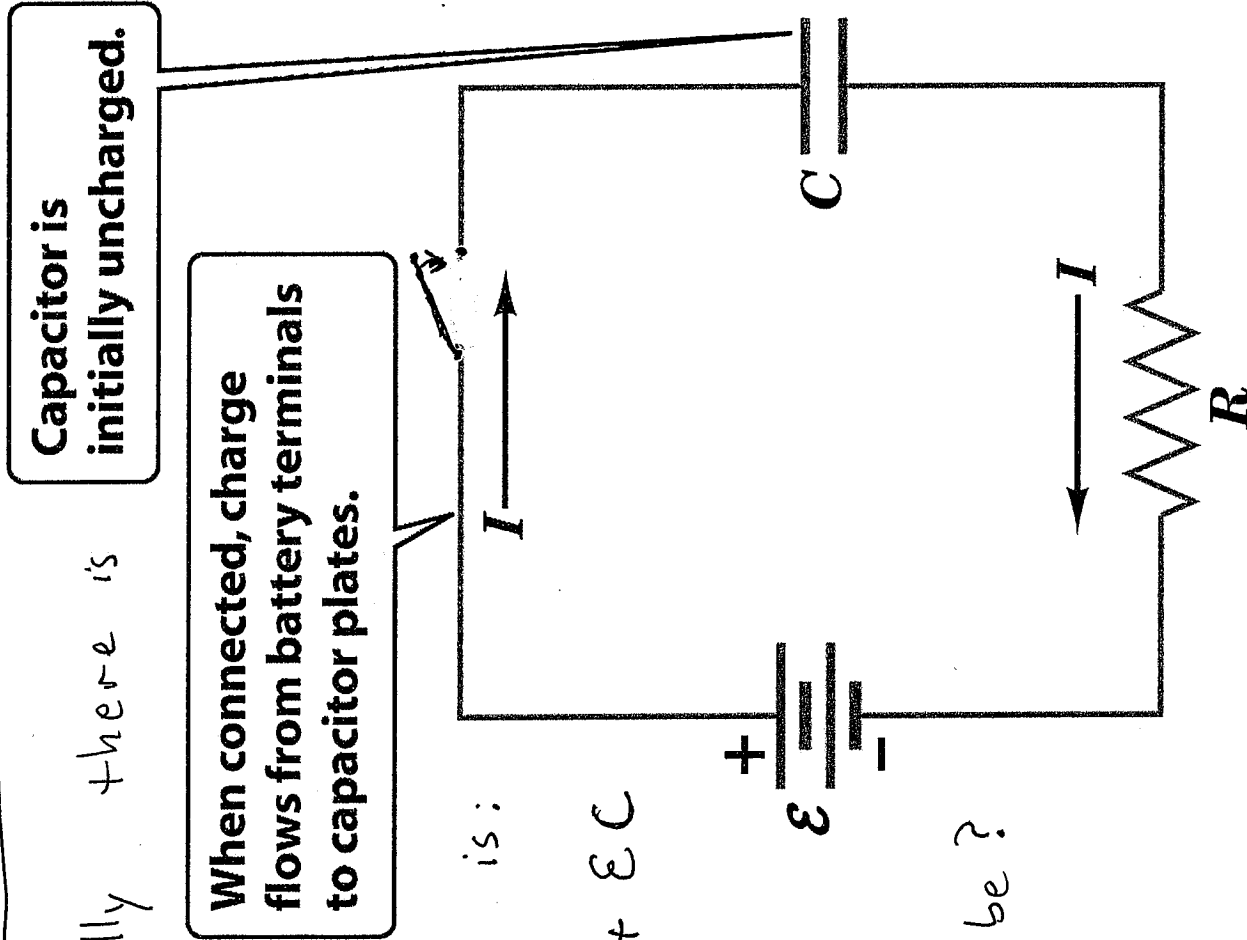


Figure 28-26 Physics for Engineers and Scientists 3/e © 2007 W. W. Norton & Company, Inc.

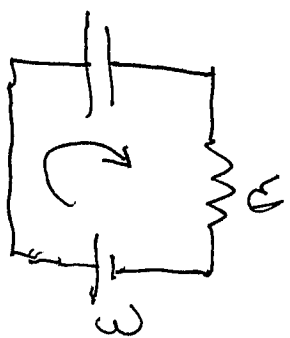Note, initially current flows as if capacitor is shorted



$$Q = C \mathcal{E} [1 - \exp(-t/RC)]$$

$$I = \frac{dQ}{dt} = \frac{\mathcal{E}}{R} \exp(-t/RC)$$

Initial current is \mathcal{E}/R .

At characteristic time $t = RC$, $I \approx 0.37 \mathcal{E}/R$.

After a long time, current approaches zero.

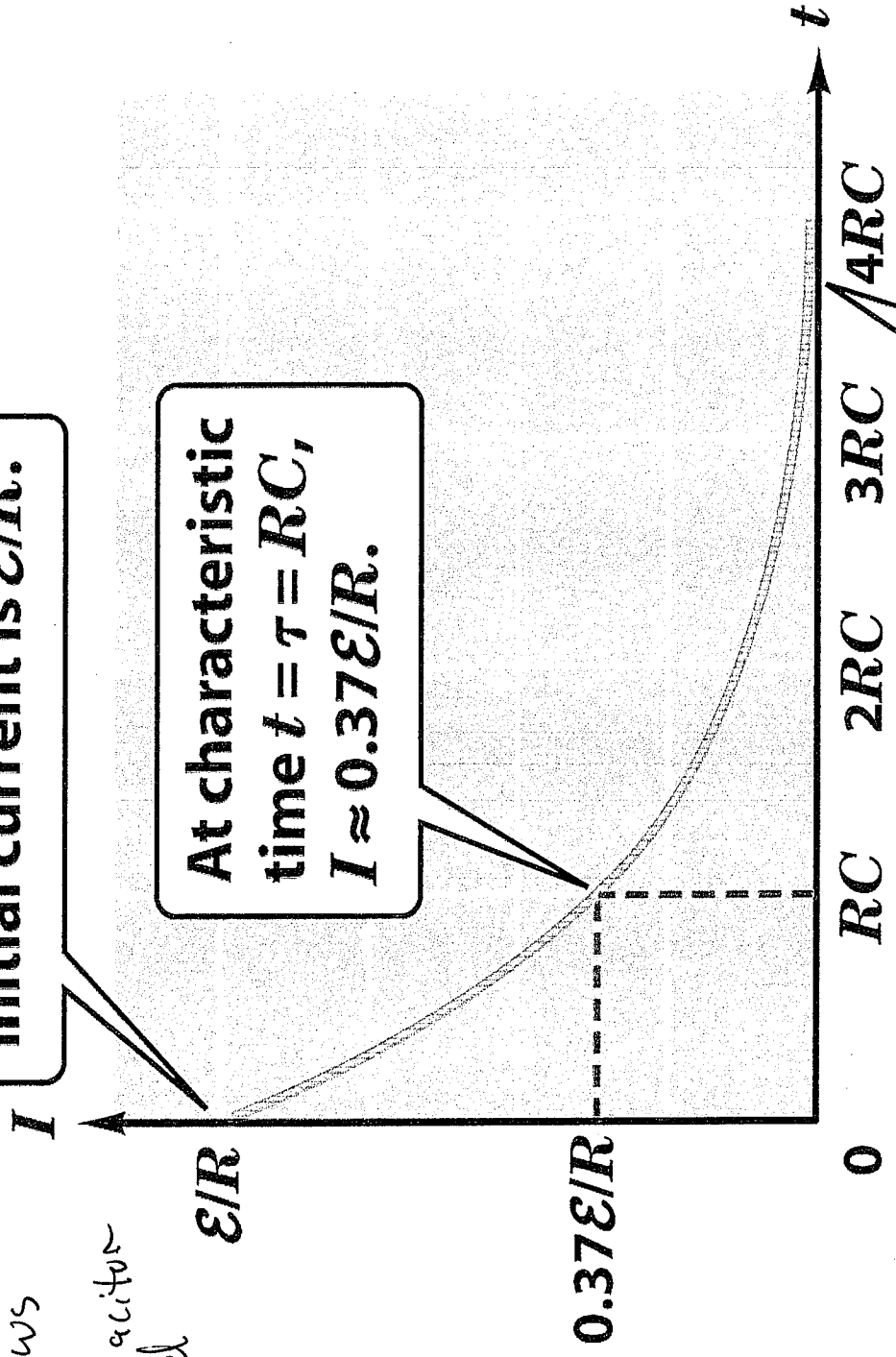


Figure 28-27b Physics for Engineers and Scientists 3/e © 2007 W. W. Norton & Company, Inc.

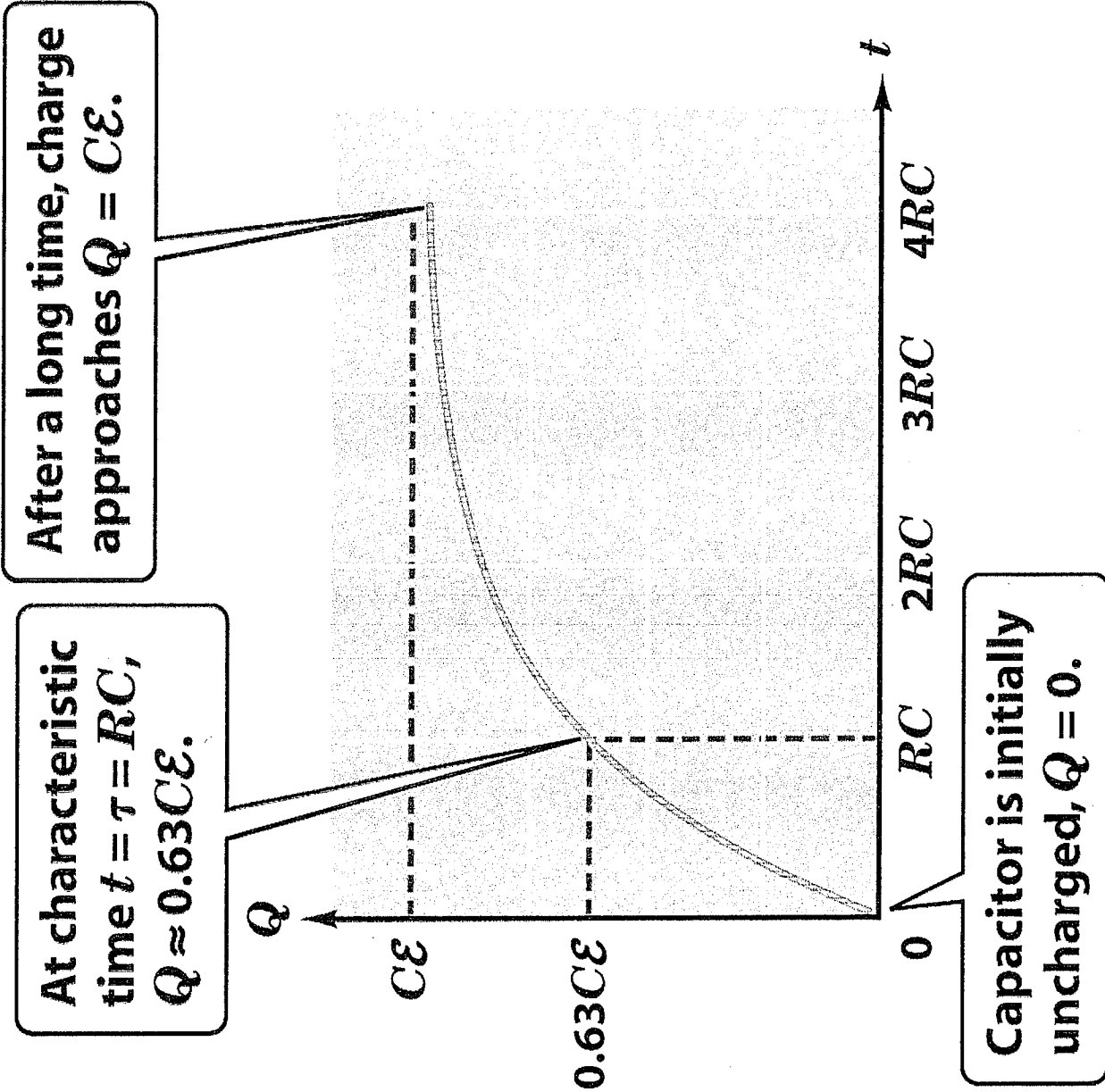


Figure 28-27a Physics for Engineers and Scientists 3/e
 © 2007 W. W. Norton & Company, Inc.

The initial voltage


across resistor

after circuit is closed is $\Delta V = ?$

(a) 0, (b) $\frac{Q_0}{C}$

The initial current, I , through the resistor after circuit is closed is

(a) $I = 0$, (b) $I = \frac{Q_0}{RC}$

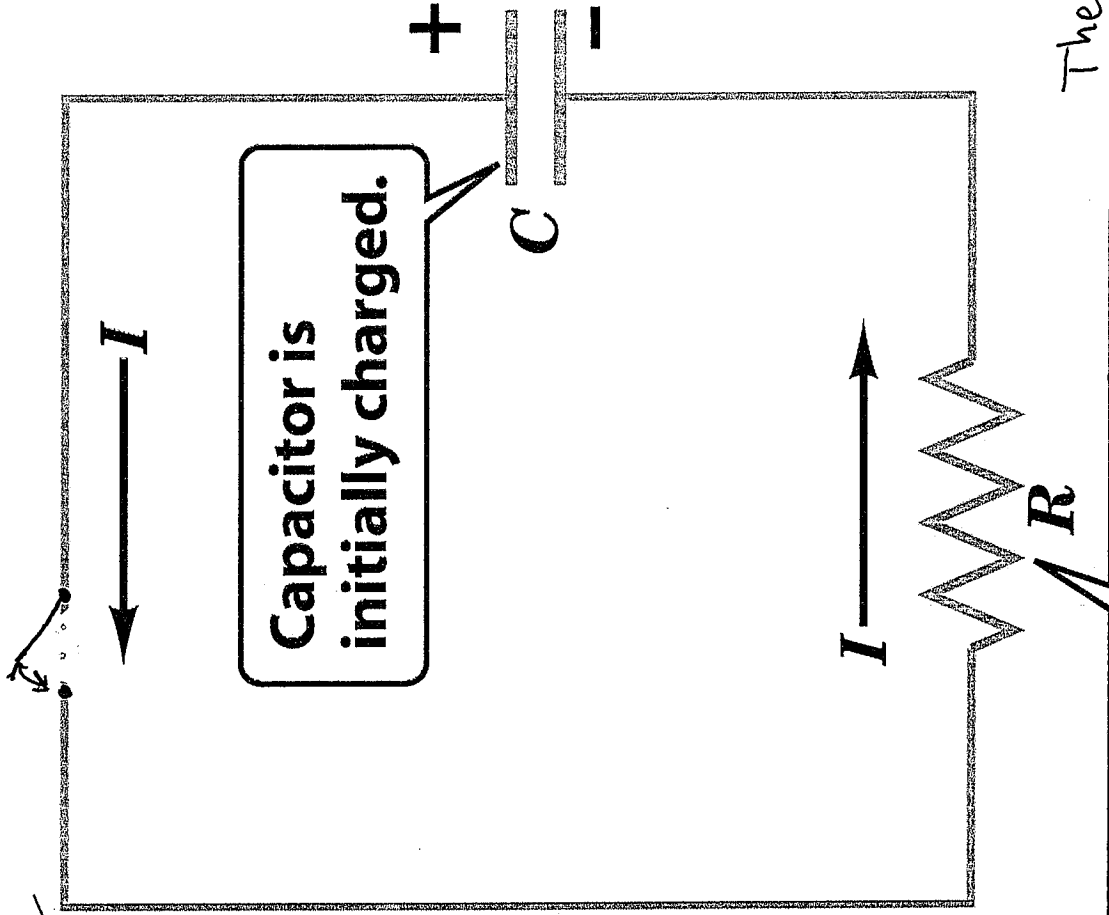

Capacitor is initially charged.

When connected, charge flows through resistor.

The final current I through the resistor is

(a) $I = 0$ (b) $I = \frac{Q_0}{RC}$

Figure 28-28 Physics for Engineers and Scientists 3/e © 2007 W. W. Norton & Company, Inc.


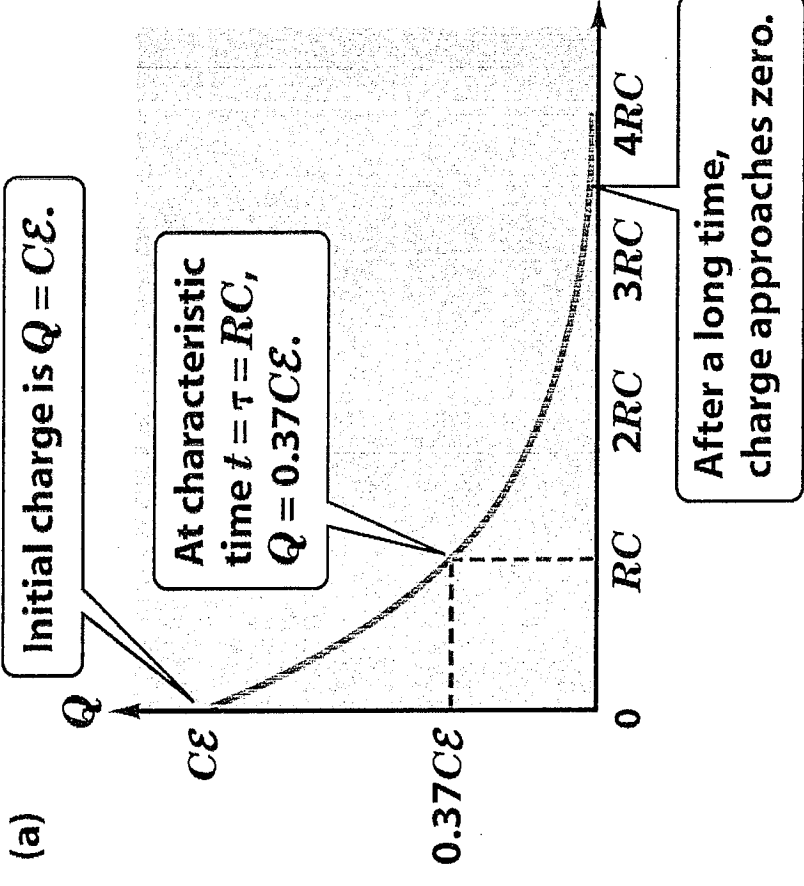
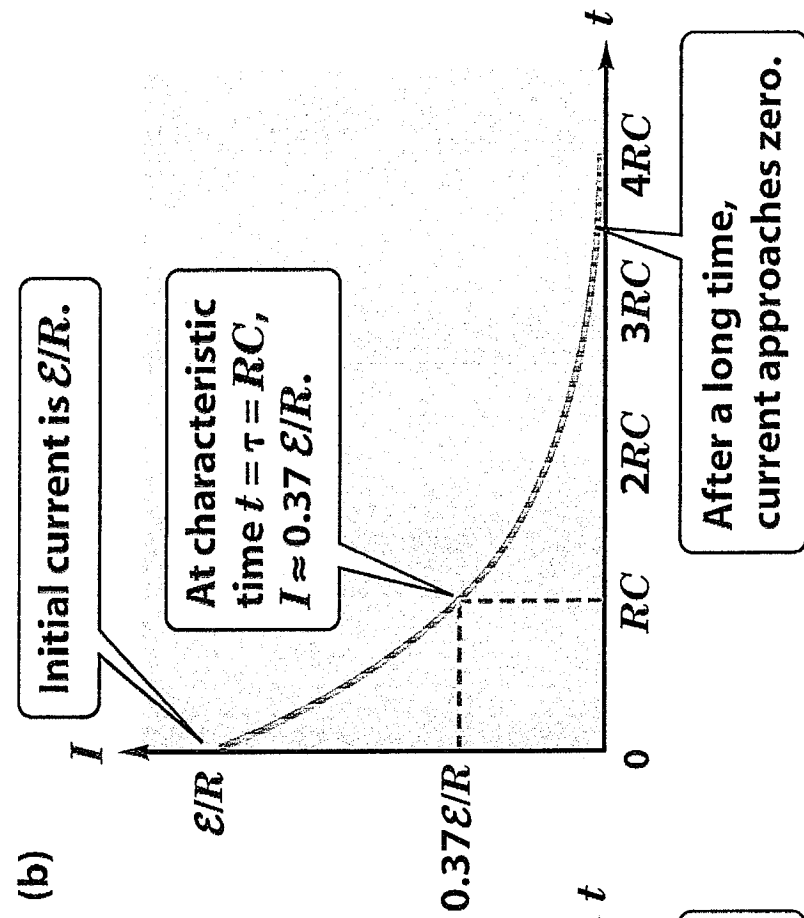


Figure 28-29 Physics for Engineers and Scientists 3/e
 © 2007 W. W. Norton & Company, Inc.

POWER DELIVERED BY A SOURCE OF emf

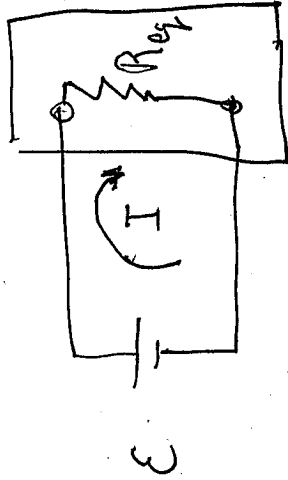


$$P = \epsilon I$$

POWER DISSIPATED BY A RESISTOR (JOULE HEAT)

$$\Delta V = IR$$
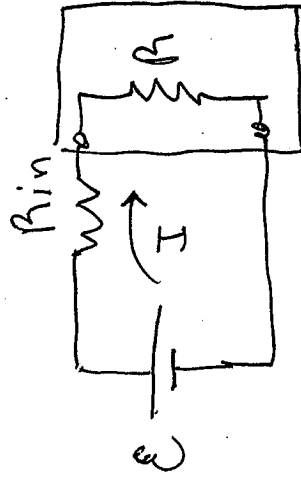
$$P_{\text{diss}} = \Delta VI = I^2 R = \frac{(\Delta V)^2}{R}$$



$$I = \frac{\mathcal{E}}{R_{in} + R}$$


$$P_{\text{diss}} = I^2 R = \frac{\mathcal{E}^2 R}{(R_{in} + R)^2}$$

$$\mathcal{E}_{\text{eff}} = \frac{P_{\text{dis}}}{P_{\text{del}}} = \frac{R}{R_{in} + R}$$

$$P_{\text{del}} = \mathcal{E} I = \frac{\mathcal{E}^2}{R_{in} + R}$$

$$P_{\text{diss}} = P_{\text{del}} \frac{R}{R_{in} + R}$$

Example of energy conservation

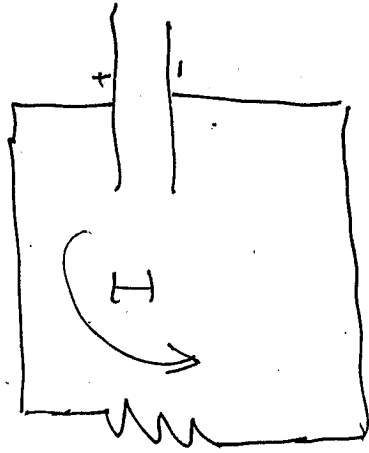

$$Q(t=0) = Q_0$$

$$\Delta V = Q(t)/C$$

Initial stored energy

$$W = \frac{1}{2} \frac{Q_0^2}{C}$$

$$\Delta V(t=0) = \frac{Q_0}{C}$$

Power dissipated

$$P = I^2 R$$

$$I(t) = \frac{\Delta V(t=0)}{R} e^{-t/RC} = \frac{Q_0}{RC} e^{-t/RC}$$


Energy dissipated = $\int_0^{\infty} P dt = \int_0^{\infty} I^2(t) R dt$

$$= \frac{R Q_0^2}{R^2 C^2} \int_0^{\infty} dt e^{-2t/RC} = \frac{Q_0^2}{2RC} \int_0^{\infty} dx e^{-x}$$

$x = \frac{2t}{RC}$

$$= \frac{Q_0^2}{2C}$$

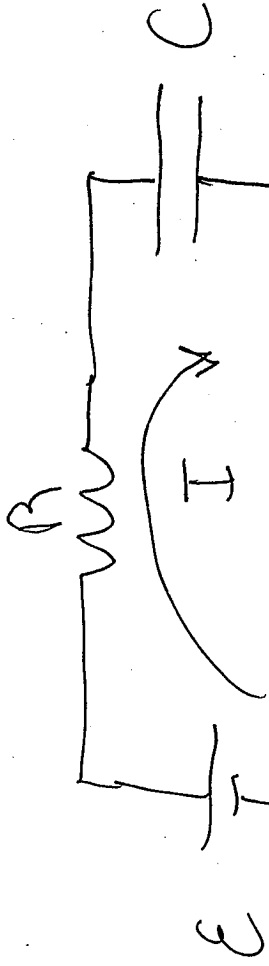How efficiently do we charge up a capacitor?



$$Q(t) = C\mathcal{E} \left[1 - \exp\left(-t/RC\right) \right]$$

$$W_C = \frac{Q^2}{2C} = \frac{\mathcal{E}^2}{2C}$$

Energy \mathcal{E} : supplied by battery

$$\text{Energy } \mathcal{E} = \int_0^\infty \mathcal{E} I(t) dt = \mathcal{E} \int_0^\infty dt \frac{dQ}{dt} = \mathcal{E} \left(Q(t=\infty) - Q(t=0) \right)$$

$$\text{Energy } \mathcal{E} = \mathcal{E}^2 / C$$


\therefore Efficiency = 50%

CHARGE ON CAPACITOR AND CURRENT IN RC CIRCUIT

when charging a capacitor

$$Q = C\mathcal{E} \left(1 - e^{-t/\tau} \right)$$
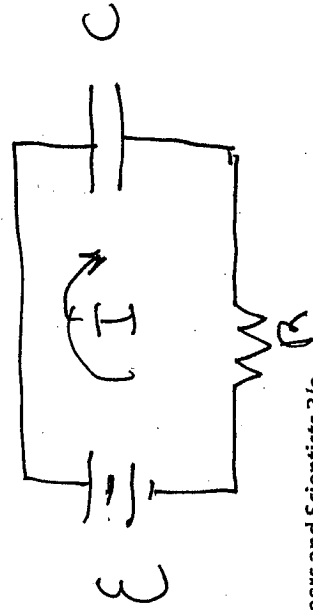
$$I = \frac{dQ}{dt} = \frac{\mathcal{E}}{R} e^{-t/\tau}$$



$$\tau = RC$$