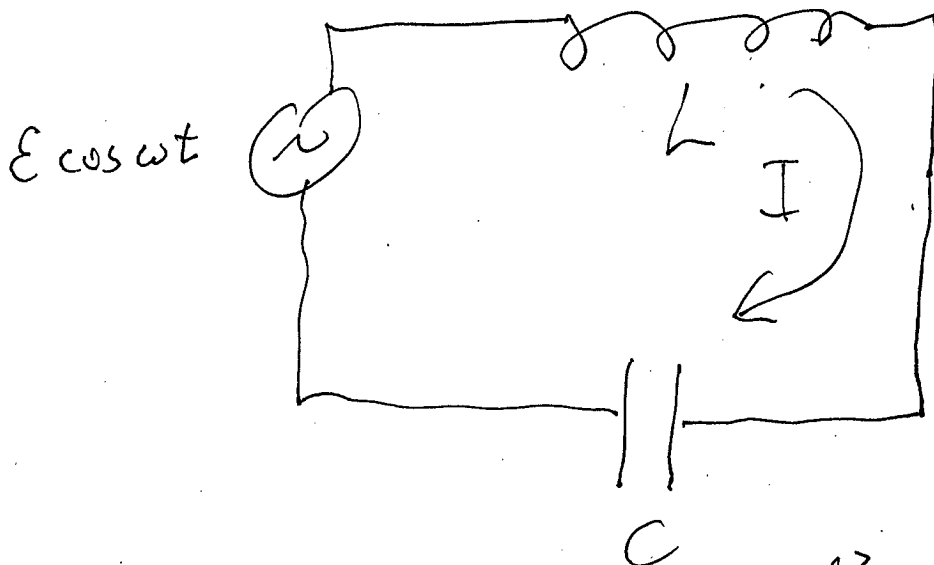


Lecture # 27

LC & RLC AC circuits

LC - series circuit



$$-E \cos \omega t + L \frac{d^2 q}{dt^2} + \frac{q}{C} = 0$$

$$I = \frac{dq}{dt} = \frac{E \sin \omega t}{\omega L - 1/\omega C} = \frac{E \sin \omega t}{X_L - X_C}$$

$X_L \equiv \omega L \equiv$ inductive impedance

$X_C \equiv \frac{1}{\omega C} \equiv$ capacitive impedance

$$= \frac{E \cos(\omega t - \frac{\pi}{2})}{\omega L - \frac{1}{\omega C}}$$


$$= \frac{E \cos(\omega t + \frac{\pi}{2})}{\frac{1}{\omega C} - \omega L}$$

$$\frac{1}{\omega C} - \omega L$$

If $\omega L > \frac{1}{\omega C}$ (high frequency), I lags V

$\frac{1}{\omega C} > \omega L$ (low frequency), V lags I
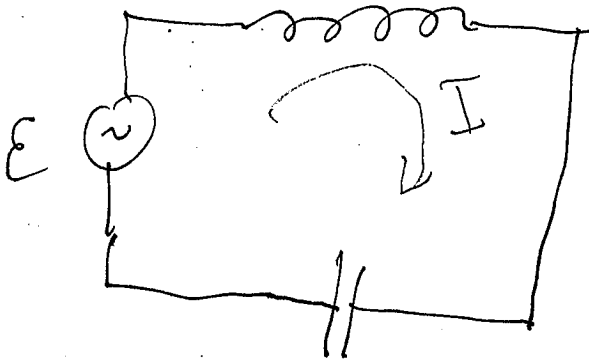
$$I = \frac{\mathcal{E} \sin \omega t}{\omega L - 1/\omega C}$$



$$\mathcal{E} = \mathcal{E}_0 \cos \omega t$$

$$I = \frac{\mathcal{E}_0 \sin \omega t}{\omega L - 1/\omega C}$$

(a) What is voltage across the inductor?

(1) $\frac{L \mathcal{E}_0 \sin(\omega t)}{\omega L - 1/\omega C}$ (b) $\frac{\mathcal{E}_0 \cos(\omega t)}{\omega(\frac{1}{\omega C} - \omega L)C}$

(c) $\frac{\mathcal{E}_0 \sin(\omega t)}{\omega(\frac{1}{\omega C} - \omega L)C}$

(d) $\frac{\omega L \mathcal{E}_0 \cos(\omega t)}{\omega L - 1/\omega C}$

(b) What is voltage across the capacitor?

In an RC AC circuit, what is the ratio of the average stored electric to magnetic energy?

stored in the circuit

electric energy stored in capacitor

$$W_E = \frac{Q^2}{2C} = \frac{(\int dt I)^2}{2C}$$

$$\omega_0^2 = \frac{1}{LC} \quad = \frac{E^2 \cos^2(\omega t - \phi)}{2\omega^2 C \left[\omega L - \frac{1}{\omega C} \right]^2} = \frac{E^2}{\omega^2 C \left[\omega L - \frac{1}{\omega C} \right]^2}$$

$$W_B = \frac{L \overline{I^2}}{2} = \frac{L}{2} \frac{E^2 \sin^2(\omega t - \phi)}{\left(\omega L - \frac{1}{\omega C} \right)^2}$$


$$= \frac{L}{4} \frac{E^2}{\left(\omega L - \frac{1}{\omega C} \right)^2}$$

$$\frac{W_E}{W_B} = \frac{\frac{E^2}{4\omega^2 C}}{\frac{L}{4} E^2} = \frac{1}{\omega^2 LC} = \frac{\omega_0^2}{\omega^2} \quad ; \quad \omega_0^2 = \frac{1}{LC}$$

$W_E > W_B$ if $\omega < \omega_0$

$W_B > W_E$ if $\omega > \omega_0$

R L C circuit

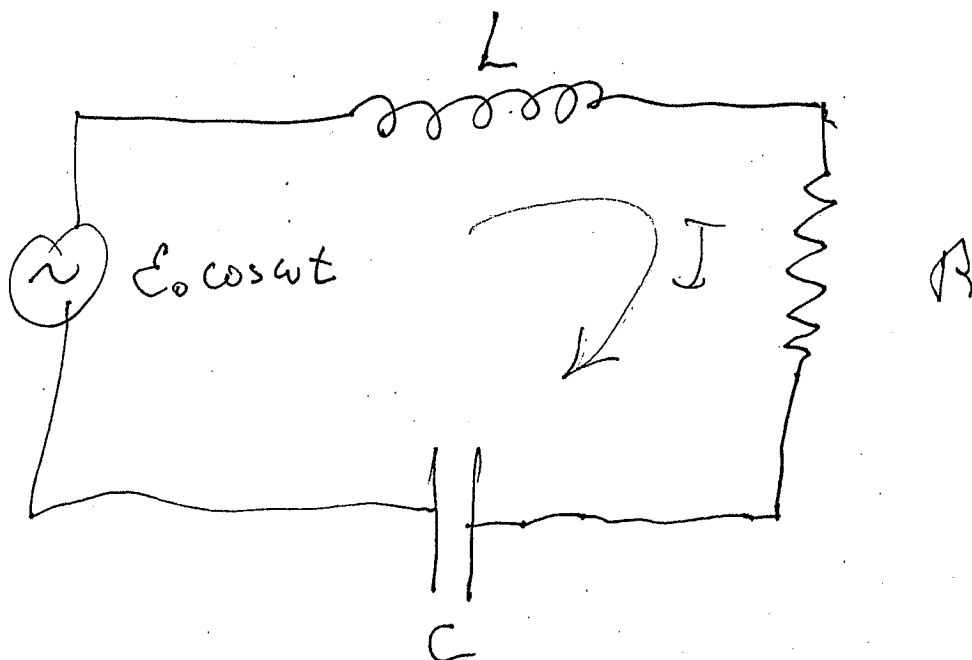

$$-E_0 \cos \omega t + L \frac{dI}{dt} + IR + \frac{\int dt' I(t')}{C} = 0$$

solution

$$I = \frac{E_0 \cos(\omega t - \psi)}{Z}$$

$$Z = \left[(\omega L - \frac{1}{\omega C})^2 + R^2 \right]^{1/2} = \text{total impedance}$$

$$\psi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

phase on current


$$-\frac{\pi}{2} < \psi < \frac{\pi}{2}$$

current
voltage

lags $X_L > X_C$

lags $X_C > X_L$

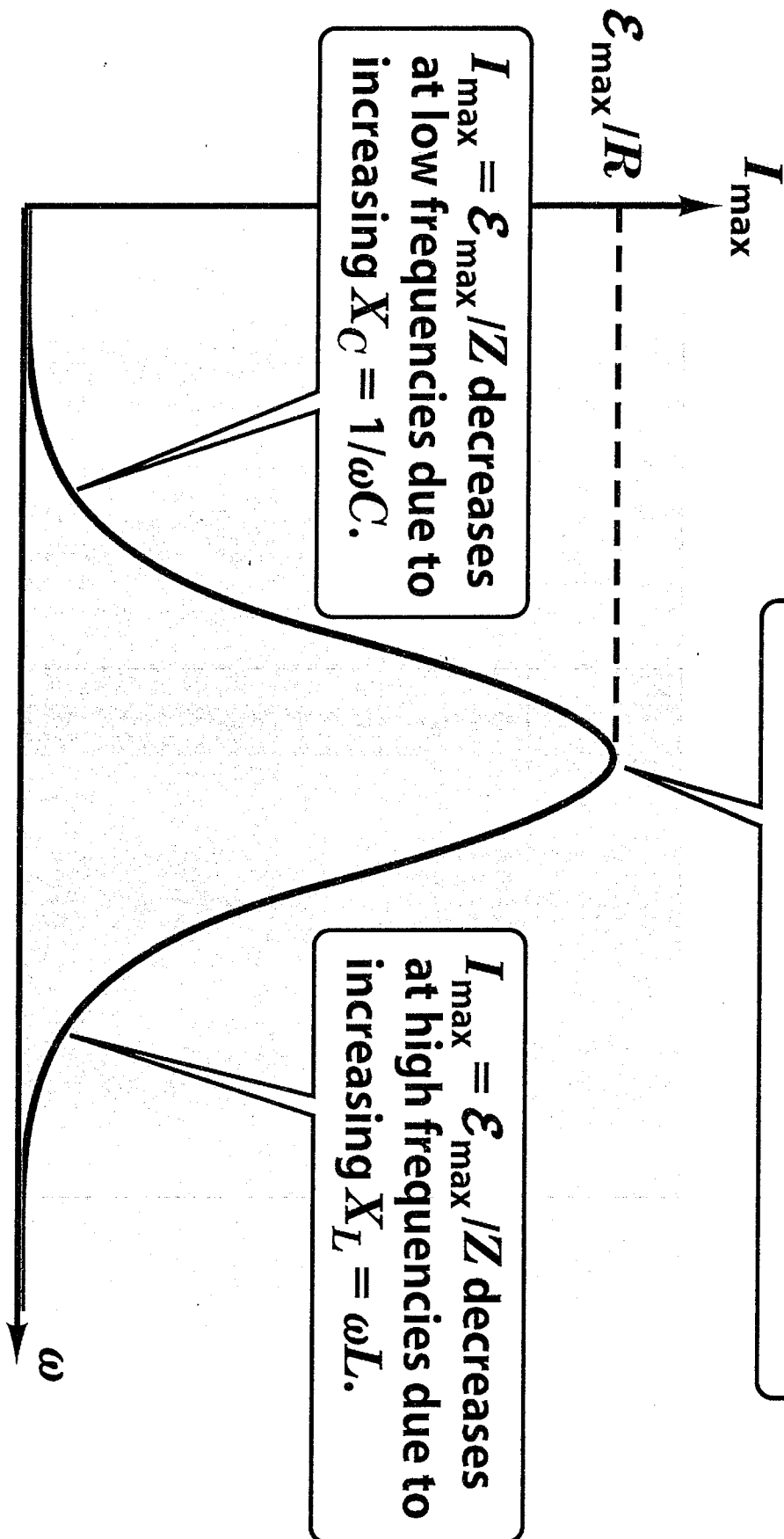Current amplitude is maximum at resonance, where capacitive and inductive reactances cancel.



$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Figure 32-29 Physics for Engineers and Scientists 3/e
© 2007 W.W. Norton & Company, Inc.

Note Impedance is smallest,
and current is largest at
frequency $\omega = \omega_0 = \frac{1}{\sqrt{LC}}$

$$\frac{L I_{rms}}{E_{rms}} = \frac{1}{\left[\left(\omega L - \frac{1}{\omega C} \right)^2 + R^2 \right]^{1/2}}$$

RMS Power Delivered by
Alternator

$$\overline{P} = \frac{1}{T} \int_0^T dt E(t) I(t)$$

$$= \frac{E_0^2}{T} \int_0^T dt \frac{\cos \omega t \cos(\omega t - \phi)}{Z(\omega)}$$


$$Z(\omega) = \left[\left(\omega L - \frac{1}{\omega C} \right)^2 + R^2 \right]^{1/2}$$

$$= \frac{E_0^2}{Z(\omega)} \left[\frac{1}{T} \int_0^T dt \cos \omega t \left(\underbrace{\cos \omega t \cos \phi}_{\frac{1}{2} \cos \phi} + \underbrace{\sin \omega t \sin \phi}_0 \right) \right]$$

$$= \frac{\cos \phi}{2 Z(\omega)} E_0^2 = \overline{P}$$

Power Delivered
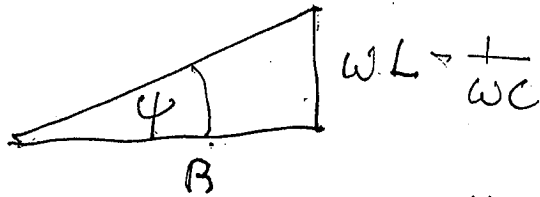
$$\bar{P} = \frac{\cos \psi E_0^2}{2 \left[\left(\omega L - \frac{1}{\omega C} \right)^2 + R^2 \right]^{1/2}}$$



$$\cos \psi = \frac{R}{\left[\left(\omega L - \frac{1}{\omega C} \right)^2 + R^2 \right]^{1/2}}$$

$$\bar{P} = \frac{R E_0^2}{2 \left[\left(\omega L - \frac{1}{\omega C} \right)^2 + R^2 \right]}$$

(Response of a resonant circuit)

If $\frac{R^2}{L^2} \ll \omega^2$, $\omega - \omega_0 \ll \omega_0$

$$\bar{P} \approx \frac{E_0^2}{2} \frac{R}{4(\omega - \omega_0)^2 L^2 + R^2}$$

$$\bar{P} = \frac{E_0^2}{2R} \frac{1}{\left(\frac{\omega - \omega_0}{\Delta \omega} \right)^2 + 1}$$

Resonance

Typical resonance function

Half width $\equiv 2\Delta\omega = \frac{R}{L}$

Quality Factor $\frac{\omega_0}{2\Delta\omega} = \frac{1}{R} \left(\frac{L}{C} \right)^{1/2}$

Difference in frequency between two points on resonance peak at half maximum power...

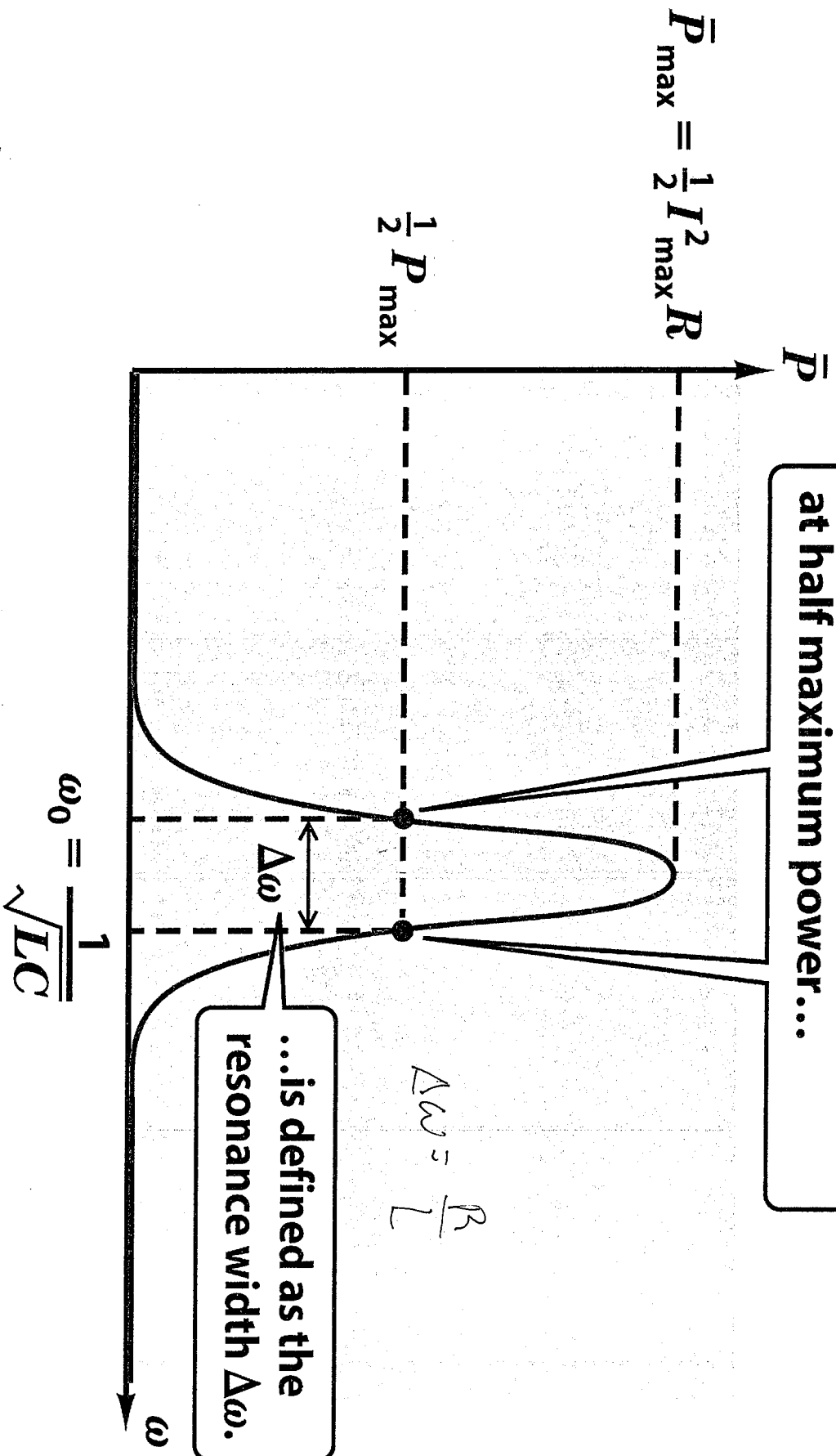


Figure 32-30 Physics for Engineers and Scientists 3/e
 © 2007 W.W.Norton & Company, Inc.